



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

ACADEMIC YEAR :2022-2023 (ODD SEMESTER)

COURSE FILE - CONTENT PAGE

| | | | |
|-----------------------|-----------------------|------------------------|---|
| YEAR & SEM | : II & III | BATCH | : 2021 -2025 |
| SUBJECT CODE | : EE3311 | SUBJECT NAME | : ELECTRICAL MACHINES LABORATORY-I |
| REGULATION | : 2021 | STAFF IN-CHARGE | :Dr.P.Narasimman |

- Syllabus
- Course plan
- Student name list
- Individual time table
- Lab Manual
- Sample Observation notebook & Record
- Model Lab
 - Question paper
 - Sample answer sheet
 - Mark statement
- Content Beyond Syllabus
- Record of Internal Mark



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SUBJECT: ELECTRICAL MACHINES LABORATORY- I

SEMESTER: III

LAB MANUAL (EE3311)
(Version:1)

PREPARED BY

Dr.P. NARASIMMAN,
AP / EEE

EE3311 ELECTRICAL MACHINES LABORATORY - I L T P C
0 0 3 1.5

SYLLABUS

1. Open circuit and load characteristics of DC shunt generator- calculation of critical resistance and critical speed.
2. Load characteristics of DC compound generator with differential and cumulative connections.
3. Load test on DC shunt motor.
4. Load test on DC compound motor.
5. Load test on DC series motor.
6. Swinburne's test and speed control of DC shunt motor.
7. Hopkinson's test on DC motor - generator set.
8. Load test on single-phase transformer and three phase transformers.
9. Open circuit and short circuit tests on single phase transformer.
10. Sumpner's test on single phase transformers.
11. Separation of no-load losses in single phase transformer.
12. Study of starters and 3-phase transformers connections.

TOTAL:45 PERIODS

P. Narayana
13/9/22

SIGNATURE OF STAFF INCHARGE

A. Anand
13/9/22
HOD/EEE



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

COURSE PLAN

| | |
|--|--|
| Sub. Code: EE3311 | Branch/Year/Sem: B.E EEE / II / III |
| Sub. Name: Electrical Machines Laboratory-I | Batch : 2021-2025 |
| Staff Name: Dr.P.Narasimman | Academic Year : 2022-23 (Odd) |

COURSE OBJECTIVE

- To expose the students to determine the characteristics of DC machines and transformers by performing experiments on these machines.
- To provide hands on experience to evaluate the performance parameters of DC machines and transformer by conducting suitable tests.

LEARNING OUTCOMES

Upon the completion of this lab, students should be able to

1. Construct the circuit with appropriate connections for the given DC machine/transformer.
2. Experimentally determine the characteristics of different types of DC machines.
3. Demonstrate the speed control techniques for a DC motor for industrial applications.
4. Identify suitable methods for testing of transformer and DC machines.
5. Predetermine the performance parameters of transformers and DC motor.
6. Understand DC motor starters and 3-phase transformer connections.

PRE-REQUISITIE

1. Knowledge about the working principles of DC Machines and Transformers.
2. Knowledge on identification of power supply source (AC or DC), ammeters voltmeters, wattmeters and their connections.

EQUIPMENTS / COMPONENTS REQUIREMENTS

1. DC Shunt Motor with Loading Arrangement
2. DC Series Motor with Loading Arrangement
3. DC compound Motor with Loading Arrangement
4. DC Shunt Motor Coupled with DC Compound Generator
5. DC Shunt Motor Coupled with DC Shunt Generator
6. DC Shunt Motor Coupled with Three phase Alternator
7. Single Phase Transformer
8. Three Phase Transformer
9. Tachometer -Digital/Analog
10. Single Phase Auto Transformer
11. Three Phase Auto Transformer
12. Single Phase Resistive Loading Bank
13. Three Phase Resistive Loading Bank

| Ex. No. | Date | Title of the Experiment | No. of Hrs. required | Cumulative No. of periods |
|------------------|------|---|----------------------|---------------------------|
| CYCLE : I | | | | |
| 1 | | Study of starters and 3-phase transformers connections. | 3 | 3 |
| 2 | | Speed control of DC shunt motor | 3 | 6 |
| 3 | | Load test on DC shunt motor | 3 | 9 |
| 4 | | Load test on DC series motor. | 3 | 12 |
| 5 | | Load test on single-phase transformer | 3 | 15 |
| 6 | | Load test on three phase transformer | 3 | 18 |
| 7 | | Swinburne's test of DC shunt motor | 3 | 21 |
| | | | | |

| CYCLE : II | | | | |
|------------|--|---|---|----|
| 8 | | Open circuit and load characteristics of DC shunt generator- calculation of critical resistance and critical speed. | 6 | 27 |
| 9 | | Load characteristics of DC compound generator with differential and cumulative connections. | 3 | 30 |
| 10 | | Load test on DC compound motor. | 3 | 33 |
| 11 | | Hopkinson's test on DC motor - generator set. | 3 | 36 |
| 12 | | Open circuit and short circuit tests on single phase transformer. | 3 | 39 |
| 13 | | Sumpner's test on single phase transformers. | 3 | 42 |
| 14 | | Separation of no-load losses in single phase transformer | 3 | 45 |

CONTENT BEYOND THE SYLLABUS

1. Load Characteristics of DC Series Generator.

Virtual Lab

<http://em-iitr.vlabs.ac.in/>

INTERNAL ASSESSMENT DETAILS

| Model | |
|----------|--------------------------|
| Portions | Cycle I & II Experiments |
| Date | |

Prepared by

P. Narasimman
13/9/22
Dr.P.Narasimman

Verified By

[Signature]
HOD/EEE 13/9/22

Approved by

[Signature]
13/9/2022
PRINCIPAL

Very files
[Signature]
EML - 5



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
Academic Year 2022-23 (ODD SEM)
Year/Sem : II/III

STUDENTS NAME LIST

| S. No. | Roll No. | Register Number | Student Name |
|--------|----------|-----------------|---------------------|
| 1 | 21EE01 | 821121105001 | ABIBHARATHI A |
| 2 | 21EE02 | 821121105002 | AKASH P |
| 3 | 21EE03 | 821121105003 | ARAVINDHAN R |
| 4 | 21EE04 | 821121105004 | DHESINGH J |
| 5 | 21EE05 | 821121105005 | GAYATHRI K C |
| 6 | 21EE06 | 821121105006 | GOKUL M |
| 7 | 21EE07 | 821121105007 | GOPINATH S |
| 8 | 21EE08 | 821121105008 | HARISHMA R |
| 9 | 21EE09 | 821121105009 | JEGADEESAN R |
| 10 | 21EE10 | 821121105010 | KARTHIKEYAN S |
| 11 | 21EE11 | 821121105011 | MEENA P |
| 12 | 21EE12 | 821121105012 | MILTON INFANT RAI P |
| 13 | 21EE13 | 821121105013 | PRAVEEN V C |
| 14 | 21EE14 | 821121105014 | RUTHRAN K |
| 15 | 21EE15 | 821121105015 | SARAVANAKUMAR M |
| 16 | 21EE16 | 821121105016 | SHANMUGAESWARAN S |
| 17 | 21EE17 | 821121105017 | SIVANANTHAM S |
| 18 | 21EE18 | 821121105018 | SIVANESAN C |
| 19 | 21EE19 | 821121105019 | SUJITHA S |
| 20 | 21EE20 | 821121105020 | SURIYA G |
| 21 | 21EE21 | 821121105021 | THAVATHEESH S |
| 22 | 21EE22 | 821121105022 | THUSARI S |
| 23 | 21EE23 | 821121105023 | VAISHNAVI V |
| 24 | 21EE24 | 821121105024 | VIDHYA M |
| 25 | 21EE25 | 821121105025 | VIJAY V |
| 26 | 21EE27 | 821121105027 | YOGESH C |
| 27 | 21EE28 | 821121105028 | YUVARAJ A |
| 28 | KL22EE01 | | MONISHAN A |
| 29 | KL22EE02 | 821121105303 | PARTHASARATHY B |
| 30 | KL22EE03 | 821121105302 | PANDIYARAJAN R |
| 31 | KL22EE04 | 821121105304 | PRAGADEESHWARAN S |
| 32 | KL22EE05 | 821121105306 | VEERASELVAN.V |
| 33 | KL22EE06 | 821121105305 | UDHAYAM.S |

R. Jimmy
 STAFF INCHARGE

A. Altham
 HOD/EEE 27/04/23



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
B.E - EEE (Reg. 2021) - With Effect from 22.8.2022 - Tentative Last working Day 08.12.22

Batch:2021 - 2025

Strength:30

Year: II Semester: III Class Room : 132 Block: I

| Session | 1 | 2 | 10.45 am | 3 | 4 | 12.30 pm | 5 | 6 | 02.40 pm | 7 | 8 | |
|---------|--------------------|--------------------|---------------|--------------------|--------------------|--------------------|--------------------|--------------------|---------------|--------------------|--------------------|--|
| Day | 09.15am 10.00am | 10.00am 10.45am | - 11.00 am | 11.00am 11.45am | 11.45am 12.30pm | - 01.10 pm | 01.10pm 01.55pm | 01.55pm 02.40pm | - 02.50 pm | 02.50pm 03.35pm | 03.35pm 04.20pm | |
| MON | CS3354 | EE3303 | | MA3303 | EE3301 | LUNCH BREAK | EE3302 | CS3363 | BREAK | CS3363 | | |
| TUE | EE3301 | MA3303 | | EC3301 | CS3354 | | EE3303 | MA3303 | | EE3302 | T & P (SS) | |
| WED | EE3302 | EE3301 | | EC3301 | LIB/NET | | MA3303 | EE3311 | | EE3311 | | |
| THU | MA3303 | EE3301 | | CS3354 | EE3302 | | EE3303 | EC3301 | | GE3361 | | |
| FRI | EE3303 | CS3354 | | EC3301 | T & P (A) | | EE3301 | EC3311 | | EC3311 | | |
| SAT | EC3301 | EE3302 | | EE3303 | EE3301 | | EE3302 | MA3303 | | CS3354 | NPTEL | |

| SUB CODE | NAME OF THE SUBJECT | CATEGORY | CREDITS | NAME OF THE STAFF | DEPT | PERIODS/WEEK |
|-------------------------------------|--|----------|---------|------------------------------------|---------|----------------|
| TUTORIAL (T), ELECTIVE (E) | | | | | | |
| MA3303 | Probability and Complex Functions | BSC | 4 | Dr.R.Geetha | Maths | 6 |
| EE3301 | Electromagnetic Fields | PCC | 4 | Ms.P.Thirumagal | EEE | 6 |
| EE3302 | Digital Logic Circuits | PCC | 3 | Mr.R.Sathyaraj | ECE | 6 |
| EC3301 | Electron Devices and Circuits | PCC | 3 | Mrs.A.Prabha | EEE | 5 |
| EE3303 | Electrical Machines-1 | PCC | 3 | Dr.P.Narasimman | EEE | 5 |
| CS3354 | Data Structure and OOPS | PCC | 3 | Mrs.S.Priyadharsini | CSE | 5 |
| EC3311 | Electronic Devices and Circuits Laboratory | PCC | 1.5 | Mrs.A.Prabha | EEE | 3 |
| EE3311 | Electrical Machines Laboratory-1 | PCC | 1.5 | Dr.P.Narasimman | EEE | 3 |
| CS3363 | Data Structure and OOPS Laboratory | PCC | 1.5 | Mrs.S.Priyadharsini | CSE | 3 |
| GE3361 | Professional Development | EEC | 1 | Mr.P.Raajeshwaran | English | 2 |
| CLASS CO-ORDINATOR | | | | NAME OF THE REPRESENTATIVES | | ROLL NO |
| Mrs.A.Prabha | | | | S.Thusari | | 22 |
| CLASS COMMITTEE CHAIR PERSON | | | | Mr.S.R.Karthikeyan | | |

| VALUE ADDITION INITIATIVES (VAI) - REGULAR HOURS | | | | | | |
|---|----------------------------------|-----|-----------------|-----|----|--|
| LIB/NET | Library / Internet | VAI | Mrs.A.Prabha | EEE | 01 | |
| NPTEL | NPTEL Swayam Courses | VAI | Mrs.A.Prabha | EEE | 01 | |
| T&P (A) | Training & Placement - Aptitude | VAI | Ms.P.Suganya | T&P | 01 | |
| T&P(SS) | Training & Placement - Softskill | VAI | Dr.B.Barankumar | T&P | 01 | |

Senthamaraj
23/8/22
DEPT. TTC

A. Mmm
23/8/22
HOD

J. Mmm
23/8/2022
PRINCIPAL



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

ACADEMIC YEAR 2022 – 2023 / ODD SEMESTER

LABORATORY MANUAL

(Version: 1)

PREPARED BY

Dr. P.NARASIMMAN, AP / EEE

Name of the Student : _____

Register Number : _____

Year / Semester : _____ **II / III** _____



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SUBJECT: ELECTRICAL MACHINES LABORATORY- I

SEMESTER: III

LAB MANUAL (EE3311)
(Version:1)

PREPARED BY

Dr.P. NARASIMMAN,
AP / EEE

EE3311 ELECTRICAL MACHINES LABORATORY - I L T P C
0 0 3 1.5

SYLLABUS

1. Open circuit and load characteristics of DC shunt generator- calculation of critical resistance and critical speed.
2. Load characteristics of DC compound generator with differential and cumulative connections.
3. Load test on DC shunt motor.
4. Load test on DC compound motor.
5. Load test on DC series motor.
6. Swinburne's test and speed control of DC shunt motor.
7. Hopkinson's test on DC motor - generator set.
8. Load test on single-phase transformer and three phase transformers.
9. Open circuit and short circuit tests on single phase transformer.
10. Sumpner's test on single phase transformers.
11. Separation of no-load losses in single phase transformer.
12. Study of starters and 3-phase transformers connections.

TOTAL:45 PERIODS

P. Narayana
12/9/22

SIGNATURE OF STAFF INCHARGE

A. Anand
13/9/22
HOD/EEE



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

COURSE PLAN

| | |
|--|--|
| Sub. Code: EE3311 | Branch/Year/Sem: B.E EEE / II / III |
| Sub. Name: Electrical Machines Laboratory-I | Batch : 2021-2025 |
| Staff Name: Dr.P.Narasimman | Academic Year : 2022-23 (Odd) |

COURSE OBJECTIVE

- To expose the students to determine the characteristics of DC machines and transformers by performing experiments on these machines.
- To provide hands on experience to evaluate the performance parameters of DC machines and transformer by conducting suitable tests.

LEARNING OUTCOMES

Upon the completion of this lab, students should be able to

1. Construct the circuit with appropriate connections for the given DC machine/transformer.
2. Experimentally determine the characteristics of different types of DC machines.
3. Demonstrate the speed control techniques for a DC motor for industrial applications.
4. Identify suitable methods for testing of transformer and DC machines.
5. Predetermine the performance parameters of transformers and DC motor.
6. Understand DC motor starters and 3-phase transformer connections.

PRE-REQUISITIE

1. Knowledge about the working principles of DC Machines and Transformers.
2. Knowledge on identification of power supply source (AC or DC), ammeters voltmeters, wattmeters and their connections.

EQUIPMENTS / COMPONENTS REQUIREMENTS

1. DC Shunt Motor with Loading Arrangement
2. DC Series Motor with Loading Arrangement
3. DC compound Motor with Loading Arrangement
4. DC Shunt Motor Coupled with DC Compound Generator
5. DC Shunt Motor Coupled with DC Shunt Generator
6. DC Shunt Motor Coupled with Three phase Alternator
7. Single Phase Transformer
8. Three Phase Transformer
9. Tachometer -Digital/Analog
10. Single Phase Auto Transformer
11. Three Phase Auto Transformer
12. Single Phase Resistive Loading Bank
13. Three Phase Resistive Loading Bank

| Ex. No. | Date | Title of the Experiment | No. of Hrs. required | Cumulative No. of periods |
|------------------|------|---|----------------------|---------------------------|
| CYCLE : I | | | | |
| 1 | | Study of starters and 3-phase transformers connections. | 3 | 3 |
| 2 | | Speed control of DC shunt motor | 3 | 6 |
| 3 | | Load test on DC shunt motor | 3 | 9 |
| 4 | | Load test on DC series motor. | 3 | 12 |
| 5 | | Load test on single-phase transformer | 3 | 15 |
| 6 | | Load test on three phase transformer | 3 | 18 |
| 7 | | Swinburne's test of DC shunt motor | 3 | 21 |
| | | | | |

| CYCLE : II | | | | |
|------------|--|---|---|----|
| 8 | | Open circuit and load characteristics of DC shunt generator- calculation of critical resistance and critical speed. | 6 | 27 |
| 9 | | Load characteristics of DC compound generator with differential and cumulative connections. | 3 | 30 |
| 10 | | Load test on DC compound motor. | 3 | 33 |
| 11 | | Hopkinson's test on DC motor - generator set. | 3 | 36 |
| 12 | | Open circuit and short circuit tests on single phase transformer. | 3 | 39 |
| 13 | | Sumpner's test on single phase transformers. | 3 | 42 |
| 14 | | Separation of no-load losses in single phase transformer | 3 | 45 |

CONTENT BEYOND THE SYLLABUS

1. Load Characteristics of DC Series Generator.

Virtual Lab

<http://em-iitr.vlabs.ac.in/>

INTERNAL ASSESSMENT DETAILS

| Model | |
|----------|--------------------------|
| Portions | Cycle I & II Experiments |
| Date | |

Prepared by

P. Narasimman
13/9/22
Dr.P.Narasimman

Verified By

[Signature]
HOD/EEE 13/9/22

Approved by

[Signature]
13/9/2022
PRINCIPAL

Very files
[Signature]
EML - 5

| | | |
|----------|--|-----------------------------------|
| Ex. No : | | STUDY OF DC MOTOR STARTERS |
| Date : | | |

AIM:

To study the working principle of DC motor starters.

NECESSITY OF STARTERS

When a supply voltage is applied to a motor the starting current is high because of very low armature resistance.

The starting current is much more than the full load current

The excessive current will blow out fuses and may damage the brushes etc

To avoid this excessive starting current, a resistance is inserted in series with the armature and is gradually cut out as the motor gains speed and develop the back e.m.f. which regulates the speed.

Equipments used for protection of dc motors, for the following reasons:


- Protect motor against damage due to short circuits in equipment
- Protect motor against damage from long-term overloads
- Protect motor against damage from excessive starting currents
- Provide a convenient manner in which to control the operating speed of motor

THREE POINT STARTER

The internal wiring for such a starter is shown in the figure. The three terminals of the starting box are marked as L, F, A. One line is directly connected to one armature terminal and one field terminal which are tied together. The other line is connected to point L which is further connected to the starting arm, through the over-current (or over load) release M.

To start the motor, the main switch is first closed and then the starting arm is slowly moved to the right. As soon as the arm makes contact with stud no.1, the field circuit is directly connected across the line and at the same time full starting resistance R_S is placed in series with the armature. The starting current drawn by the armature $= V / (R_A + R_S)$ where R_S is the starting resistance. As the arm is further moved, the starting resistance is gradually cut out till, when the arm reaches the running position, the resistance is all cut out. The arm moved over the various studs against a strong spring which tends to restore it to OFF position. There is a soft iron piece S attached and held by an electromagnet E energized by the shunt current. It is variously known as "HOLD-ON" coil, LOW-VOLTAGE (or NO-VOLTAGE) realize.

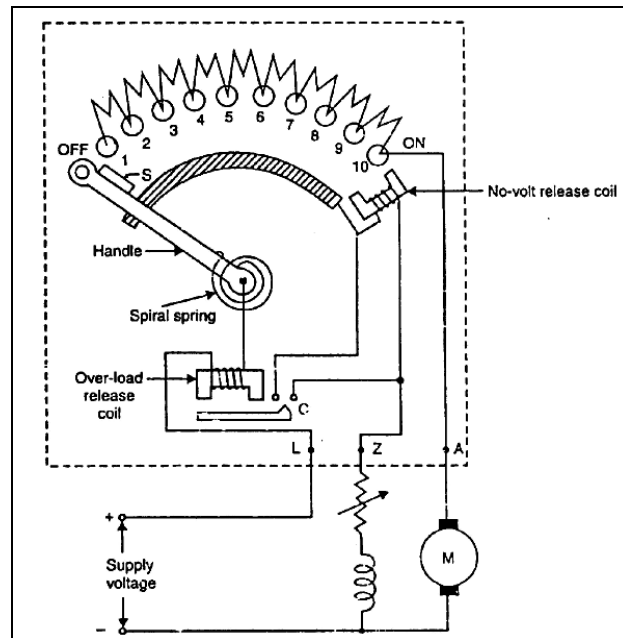It will be seen that as the arm is moved from stud 1 to the last stud, the field current has to travel back through that portion of the starting resistance that has been cut out of the armature circuit. This results in slight decrease of shunt current. But as the value of starting resistance is very small as compared to shunt field resistance, this slight decrease in I is negligible.



Three Point Starter

The normal function of HOLD-ON coil is to hold the arm in the full running position when the motor is in running position. But, in case of failure or disconnecting of the supply or break in the field circuit, it is de-energized thereby releasing the arm which is pulled back by the spring to the OFF position. This prevents the stationary armature from being put across the lines again when the supply is restored after temporary shutdown. This would have happened if the arm were left in the full null position. One great advantage of connecting the HOLD-ON coil in series with the shunt field is that, should the field circuit become open, the starting arm immediately springs back to the OFF position thereby preventing the motor from running away.


The over-current release consists of electromagnet connected in the supply line. If the motor becomes over-loaded beyond a certain predetermined value, then D is lifted and short-circuits the electromagnet. Hence, the arm is released and returns to OFF position.

The form of over-load protection described above is becoming obsolete, because it cannot be made either as accurate or as reliable as a separate well-designed circuit breaker with a suitable time element attachment. Many a times a separate magnetic contractor with an overload relay is also used.

Often the motors are protected by thermal overload relay in which a bimetallic strip is heated by the motor is itself heating up. Above a certain temperature, this relay trips and opens the line contractor thereby isolating the motor from the supply.

It is desired to control the speed the motor in addition, and then a field rheostat is connected in the field circuit as shown in the figure. The motor speed can be increased by weakening the flux ($N \propto 1/\phi$) obviously, there is a limit to the speed increase obtained in this way, although speed ranges of three or four are possible. If too much resistance is 'cut-in' by the field rheostat, then field current is reduced very much so that it is unable to create enough electromagnetic pull to overcome the spring tension. Hence, the arm is pulled back to OFF position. It is this undesirable feature of a three-point starter which makes it unsuitable for use with variable speed motors. This has resulted in wide range application of four point starters.

FOUR POINT STARTER

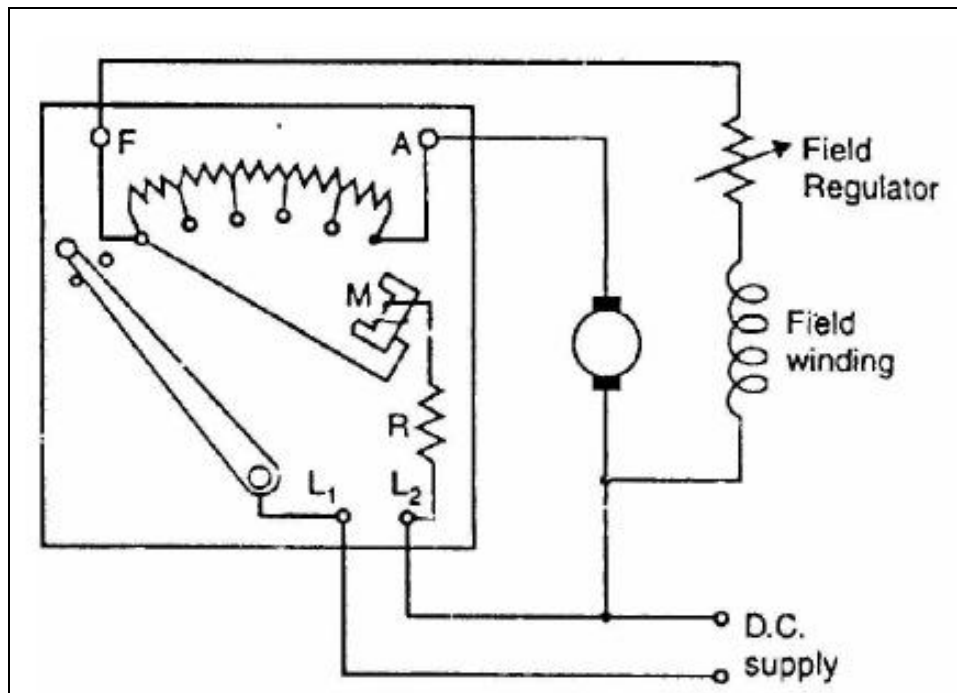

Such a starter with its internal winding is shown connected to a long-shunt compound motor in fig4. when compared to the three-point starter, it will be noticed that one important change has been made i.e., the HOLD-ON coil has been taken out of the shunt field and has been connected directly across the line through a protecting resistance as shown. When the arm touches stud no.1, then the line current divides into three parts,

- One part passes through starting resistance R_s , series field and motor armature
- The second part passes through the shunt field and its field rheostat.
- The third part passed through the HOLD-ON coil and current protecting resistance R .

It should be particularly noted that with this arrangement any change of current in the shunt field circuit does not at all affect the current passing through the HOLD-ON coil because the two circuits are independent of each other. It means that the electromagnetic pull exerted by the HOLD-ON coil will always be sufficient and will prevent the spring from restoring the starting arm to OFF position no matter how the field rheostat or regulator is adjusted.

RESULT:

Thus the working principle of DC motor starters were studied.

VIVA QUESTIONS:

1. What is a starter?
2. What is the necessity of starter?
3. Classify the DC motor starters.
4. What is the main disadvantage of 3 point starter?
5. What are the advantages of using starters?

Ex. No :

OPEN CIRCUIT & LOAD CHARACTERISTICS OF DC SHUNT GENERATOR - CRITICAL RESISTANCE & CRITICAL SPEED


Date :

AIM:

To draw the open circuit and load characteristics of self excited DC shunt generator by conducting open circuit test and load test on it.

APPARATUS REQUIRED:

| S.NO. | APPARATUS REQUIRED | TYPE | RANGE | QUANTITY |
|-------|--------------------|-----------------|--------------------------------|----------|
| 1 | Ammeter | Moving coil(MC) | (0-2)amps, (0-5)amps | Each 1 |
| 2 | Ammeter | Moving coil(MC) | (0-20)amps | 1 |
| 3 | Voltmeter | Moving coil(MC) | (0-10)volts | 1 |
| 4 | Voltmeter | Moving coil(MC) | (0-300)volts | 1 |
| 5 | Rheostat | Wire wound | 230 ohms/1.7amps | 1 |
| 6 | Rheostat | Wire wound | 300 Ω /2amps, 50/5 amps | Each 1 |
| 7 | Resistive load | - | 3kilo watts (kw) | 1 |
| 8 | Tachometer | Digital | - | 1 |
| 9 | Connecting wires | - | - | Required |

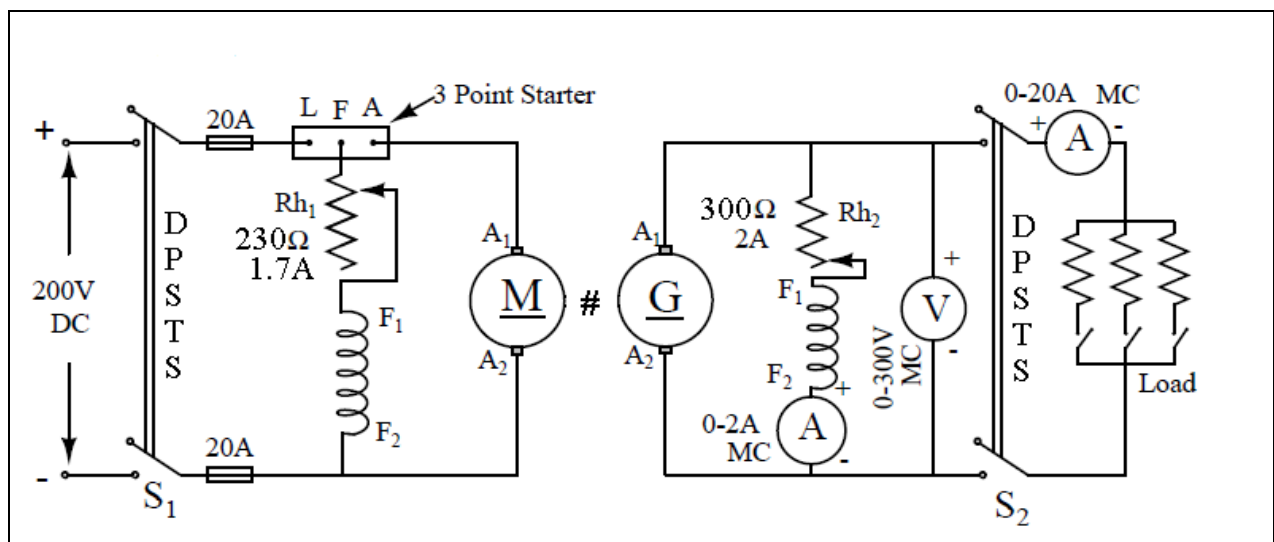CIRCUIT DIAGRAM:


Circuit diagram for open circuit and load characteristics of DC Shunt generator

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | DC SHUNT MOTOR | DC SHUNT GENERATOR |
|--------------------|----------------|--------------------|
| Rating(kw) | | |
| Voltage(volts) | | |
| Current(amps) | | |
| Speed(rpm) | | |
| Excitation volt | | |
| Excitation Current | | |

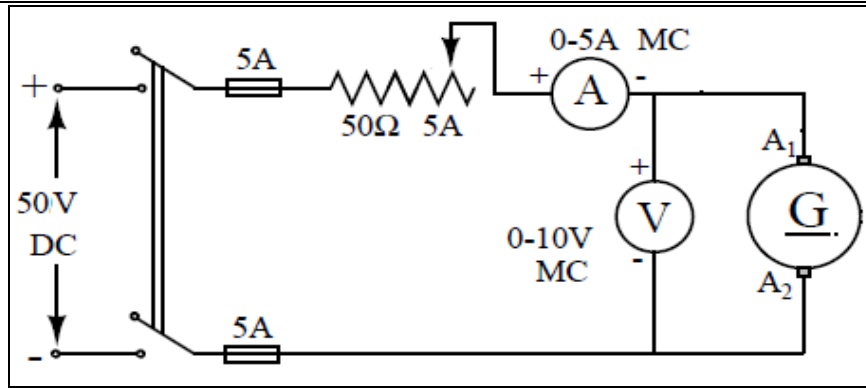

Circuit Diagram to find the Armature Resistance.

FORMULA:

$$E_g = V + I_a R_a \text{ (volts)}$$

$$I_L = I_a + I_f \text{ (amps)}$$

$$R_a = \frac{V_a}{I_a} \text{ (ohm)}$$

Where

E_g - Generated emf at load condition in volts V - Terminal voltage in volts

I_a - Armature current in ohm

I_L - Load current in amps

I_f - Field current in amps

V_a - Armature voltage in volts

PRECAUTIONS:

- All the (Double pole single through) DPST switch should be kept open
- Motor field rheostat should be in minimum position only
- Generated field rheostat should be in maximum position only
- All the switches in resistive load should be in off position
- In the measurement of armature resistance, rheostat should be in maximum resistance position.

PROCEDURE:**A. OPEN CIRCUIT TEST:**

1. Make the connection as per the circuit diagram
2. Close the (Double pole single through) DPST switch
3. Start the motor using three point starter.
4. By adjusting motor field rheostat set the motor-generator to its rated speed
5. Note down the generator voltage indicated by the voltmeter in table.
6. Adjust the generator field rheostat and note down the field current (I_f) & generator emf (E_o) indicated by the ammeter and voltmeter respectively
7. Repeat the same procedure until the voltmeter reads rated voltage of dc shunt Generator and determine the critical resistance value.

TABULATION FOR OPEN CIRCUIT TEST ON DC SHUNT GENERATOR

| S.No. | Field current I_f in amps | Generated emf E_o in volts |
|-------|-----------------------------|------------------------------|
| | | |
| | | |
| | | |
| | | |
| | | |

B. LOAD TEST:



1. Now close the (Double pole single through) DPST switch.
2. Adjust the resistive load and note down the corresponding load current I_L and terminal voltage indicated by the ammeter and voltmeter respectively.
3. Repeat the same procedure till the load current reaches the rated load current.

TABULATION FOR LOAD TEST ON DC SHUNT GENERATOR


| S.No. | Load current (I_L in amps) | Terminal voltage (V_t in volts) | Armature current (I_a in amps) | Generated voltage (E_g in volts) |
|-------|-------------------------------|------------------------------------|-----------------------------------|-------------------------------------|
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

FIND THE ARMATURE RESISTANCE

| S.No | Armature Current (I_a) (amps) | Armature Voltage (V_a) (volts) | Armature Resistance $R_a = V_a / I_a$ (ohms) |
|------|-----------------------------------|------------------------------------|--|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

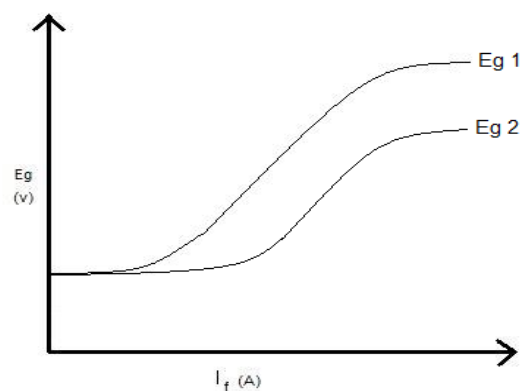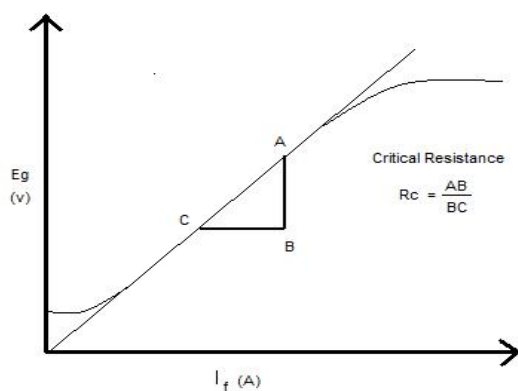MODEL GRAPH:**Find out the Critical Resistance open circuit characteristics**

Graph Representing the Magnetization or Open Circuit of Self Excited DC Shunt Generator.

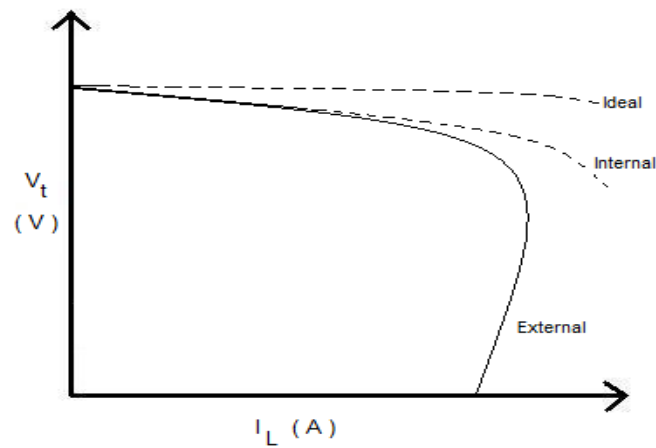Load Characteristics

Graph Representing The Load Characteristics of Self Excited DC Shunt Generator.

CALCULATIONS:**RESULT:**

Thus the open circuit and load characteristics test was conducted on DC Shunt generator and the performance curves were drawn.

VIVA QUESTIONS:

1. What is the standard direction of rotation of a DC generator?
2. What is meant by voltage buildup of a generator?
3. What is critical resistance of a shunt generator? How it is determined?
4. What do you mean by critical speed of a shunt generator?
5. Why is the resistance of the field winding of a DC Shunt generator kept below the critical field resistance?


| | | |
|----------|--|---|
| Ex. No : | | LOAD CHARACTERISTICS OF DC COMPOUND GENERATOR WITH DIFFERENTIAL AND CUMULATIVE CONNECTIONS |
| Date : | | |

AIM:

To draw the open circuit and load characteristics of DC Compound generator by conducting open circuit test and load test on it.

APPARATUS REQUIRED:

| S.NO. | APPARATUS REQUIRED | TYPE | RANGE | QUANTITY |
|-------|--------------------|-----------------|---------------------------------|----------|
| 1 | Ammeter | Moving coil(MC) | (0-2)amps,(0-5)amps | Each 1 |
| 2 | Ammeter | Moving coil(MC) | (0-20)amps | 1 |
| 3 | Voltmeter | Moving coil(MC) | (0-10)volts | 1 |
| 4 | Voltmeter | Moving coil(MC) | (0-300)volts | 1 |
| 5 | Rheostat | Wire wound | 300 ohms/2amps, 5 ohms/5amps | Each 1 |
| 6 | Rheostat | Wire wound | 300 ohms, 2amps | 1 |
| 7 | Resistive load | - | 3 kilowatts(kw) | 1 |
| 8 | Tachometer | Digital | - | 1 |
| 9 | Connecting wires | - | - | Req |

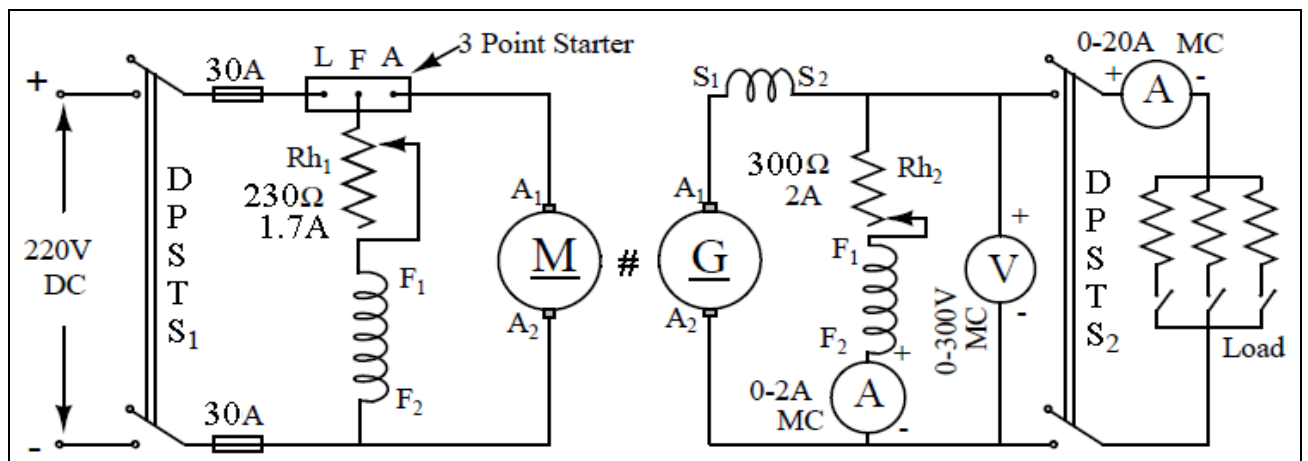
CIRCUIT DIAGRAM:

DC Compound Generator - Cumulative

NAME PLATE DETAILS**FUSE RATING:**

For Load Test Fuse Rating=125% of rated current.

| PARAMETER | DC SHUNT MOTOR | DC COMPOUND GENERATOR |
|--------------------|----------------|-----------------------|
| Rating(kw) | | |
| Voltage(volts) | | |
| Current(amps) | | |
| Speed(rpm) | | |
| Excitation volt | | |
| Excitation Current | | |

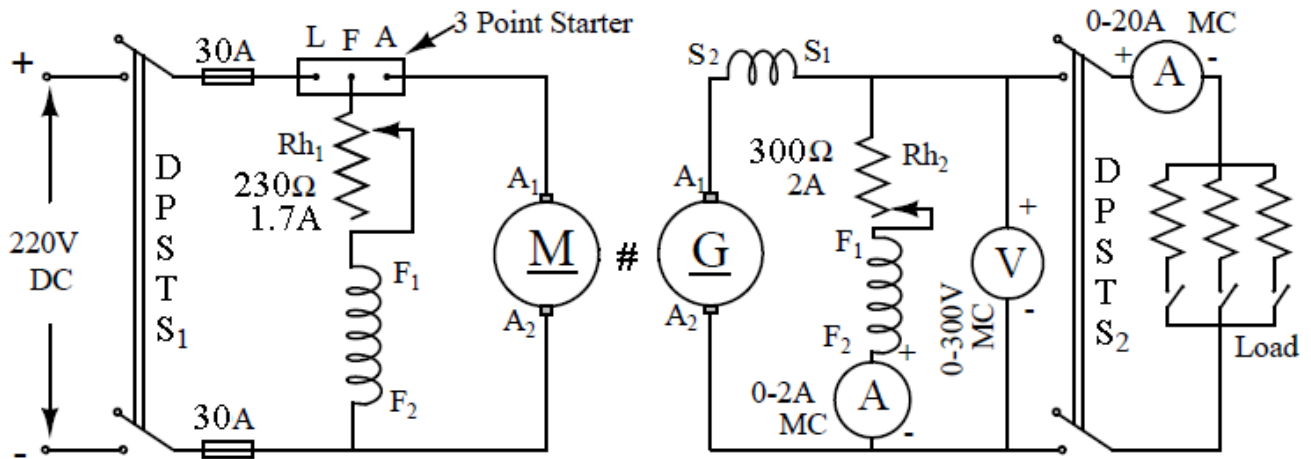

DC Compound Generator - Differential

PRECAUTIONS:

- All the (Double pole single through) DPST switch should be kept open
- Motor field rheostat should be in minimum position only
- Generated field rheostat should be in maximum position only
- All the switches in resistive load should be in off position
- In the measurement of armature resistance, rheostat should be in maximum resistance position.

PROCEDURE:**LOAD TEST (Cumulative Compound) :**

1. Now close the (Double pole single through) DPST switch.
2. Adjust the resistive load and note down the corresponding load current I_L and terminal voltage indicated by the ammeter and voltmeter respectively.
3. Repeat the same procedure till the load current reaches the rated load current.

TABULATION FOR LOAD TEST OF DC CUMULATIVE COMPOUND GENERATOR


| S.No. | Load current (I_L in amps) | Terminal voltage (V_t in volts) |
|-------|-------------------------------|------------------------------------|
| | | |
| | | |
| | | |
| | | |
| | | |

LOAD TEST (Differential Compound) Series winding terminal S1 & S2 are interchanged

1. Now close the (Double pole single through) DPST switch.
2. Adjust the resistive load and note down the corresponding load current I_L and terminal voltage indicated by the ammeter and voltmeter respectively.
3. Repeat the same procedure till the load current reaches the rated load current.

TABULATION FOR LOAD TEST OF DC DIFFERENTIAL COMPOUND GENERATOR

| S.No. | Load current (I_L in amps) | Terminal voltage (V_t in volts) |
|-------|----------------------------------|--|
| | | |
| | | |
| | | |
| | | |
| | | |

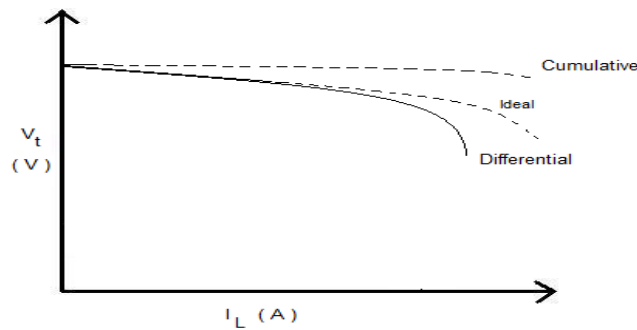MODEL GRAPH:

Graph representing the load characteristics of DC compound Generator.

RESULT:

Thus the open circuit and load test was conducted and the performance curves were drawn.

VIVA QUESTIONS:

1. What is the location of series field winding in a compound generator?
2. What is the necessity of compound generator?
3. Why do we use over-compounded generators in power stations?
4. What happens if a dc machine is operated at a speed below the rated speed?
5. Can a dc machine be operated under conditions different from those on the name plate?

Ex. No :

Date :

LOAD TEST ON DC SHUNT MOTOR


AIM:

To conduct the load test on a given DC shunt motor and to draw its performance curves.

APPARATUS REQUIRED:

| S.No | Name of the apparatus | Type | Range | Quantity |
|------|-----------------------|-----------------|-----------------|----------|
| 1 | Ammeter | Moving coil(MC) | (0-20) amps | 1 |
| 2 | Voltmeter | Moving coil(MC) | (0-300) volts | 1 |
| 3 | Rheostat | Wire wound | 230ohms,1.7amps | 1 |
| 4 | Tachometer | Digital | - | 1 |
| 5 | Connecting wires | - | - | Req |

CIRCUIT DIAGRAM:

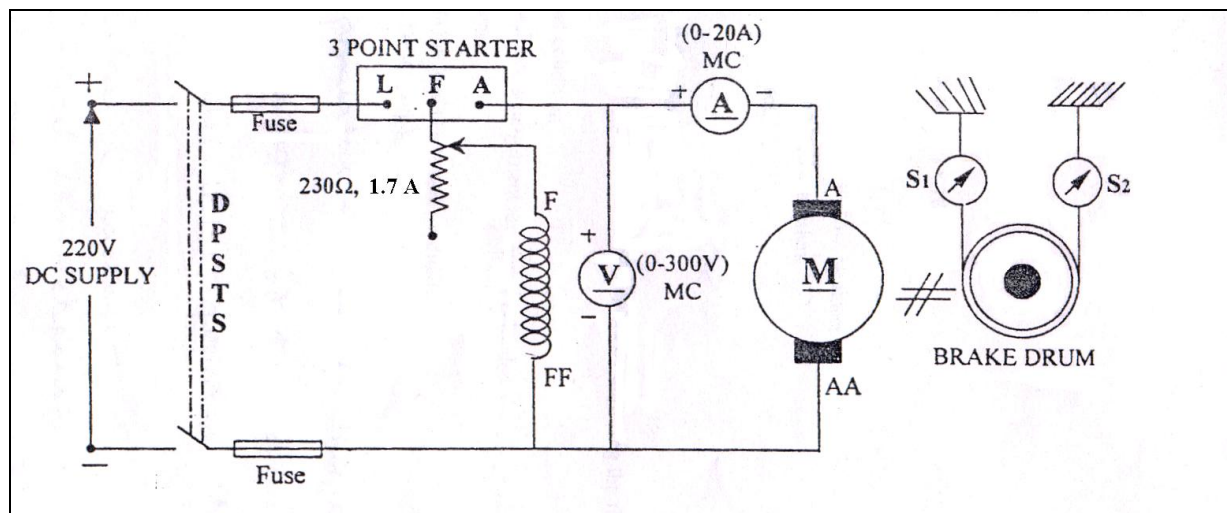

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

FORMULA:

$$\text{Torque, } T = (S_1 - S_2) \times \left(R + \frac{t}{2}\right) \times 9.81 \text{ Nm.}$$

Where R -radius of brake drum in m.

t - thickness of the belt in m.

S_1, S_2 -spring balance reading in Kg.

Input Power, $P_i = V_L I_L$ Watts, Where, V_L -load voltage in volts, I_L -load current in amps

Output Power, $P_o = \frac{2\pi NT}{60}$ Watts, Where, N -Speed of the armature in rpm, T -Torque in Nm.

$$\% \text{ Efficiency} = \frac{\text{Output Power}}{\text{Input Power}} \times 100$$

NAME PLATE DETAILS

| PARAMETER | DC SHUNT MOTOR |
|----------------|----------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

PRECAUTIONS:

- The motor field rheostat should be kept at minimum resistance position.
- At the time of starting the motor should be in no load condition.
- The motor should be run in anticlockwise direction.

PROCEDURE:


1. Connections are given as per the circuit diagram.
2. Using the three point starter the motor is started to run at the rated speed by adjusting the field rheostat if necessary.
3. The meter readings are noted at no load condition.
4. By using the break drum with spring balance arrangement the motor is loaded and the corresponding readings are noted up to the rated current.
5. After the observation of all the readings the load is released gradually.
6. The motor is switched off.

TABULATION


OBSERVATION: Radius of a brake drum= m

| S.No | V _a (volts) | I _L (amps) | I _F (amps) | N(rpm) | Spring Balance | | S ₁ - S ₂ (kg) | Torque (Nm) | Input(watts) | Output (watts) | Efficiency %η |
|------|---------------------------|--------------------------|--------------------------|--------|----------------|----------------|---|----------------|------------------|-------------------|------------------|
| | | | | | S ₁ | S ₂ | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |


MODEL GRAPH:

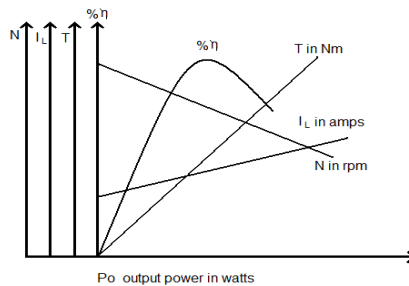

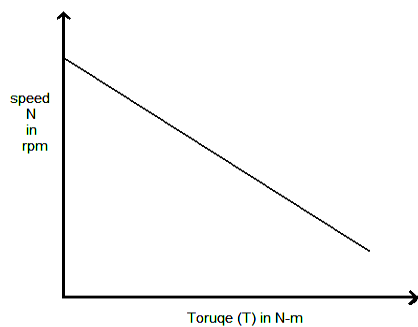Graph Representing the Load Characteristics of DC Shunt Motor.



Mechanical Characteristics

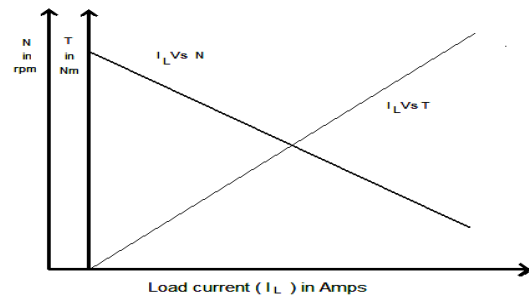

Electrical Characteristics

CALCULATIONS:**RESULT:**

Thus the load test was conducted on DC Shunt motor and the performance curve was drawn.

VIVA QUESTIONS:

1. How may the direction of rotation of a dc motor be reversed?
2. What will happen if both armature and field currents are reversed?
3. What will happen if both currents are reversed?
4. What happens when a dc shunt motor is connected across an ac supply?
5. What will happen if a shunt motor is directly connected to the supply line?


| | | |
|----------|--|---------------------------------------|
| Ex. No : | | LOAD TEST ON DC COMPOUND MOTOR |
| Date : | | |

AIM:

To conduct load test on DC compound motor and to draw its performance characteristics.

APPARATUS REQUIRED:

| S.No | Name of the Equipment | Type | Range | Quantity |
|------|-----------------------|------------------|-----------------|-------------|
| 1 | DC compound motor | - | - | 1 |
| 2 | Rheostat | Wire Wound | 230ohms/1.7amps | 1 |
| 3 | Voltmeter | Moving coil (MC) | (0-300) volts | 1 |
| 4. | Ammeter | Moving coil(MC) | (0-20) volts | 1 |
| 5 | Connecting wires | - | - | As required |

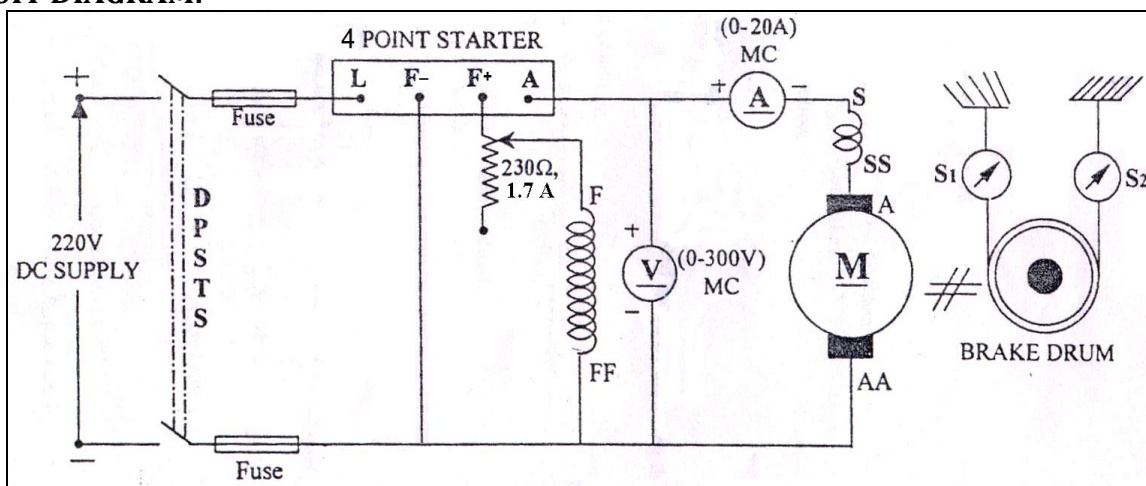CIRCUIT DIAGRAM:**FUSE RATING:**

For Load Test Fuse Rating=125% of rated current.

FORMULA :

$$\text{Torque, } T = (S_1 - S_2) \times \left(R + \frac{t}{2}\right) \times 9.81 \text{ Nm}$$

Where R -radius of brake drum in m

t - thickness of the belt in m

S_1, S_2 -spring balance reading in Kg

$$\text{Input Power, } P_i = V_L I_L \text{ Watts}$$

Where V_L -load voltage in volts

I_L -load current in amps

$$\text{Output Power, } P_o = \frac{2\pi NT}{60} \text{ Watts}$$

Where N -Speed of the armature in rpm

T -Torque in N-m

$$\% \text{ Efficiency} = \frac{\text{Output Power}}{\text{Input Power}} \times 100$$

NAME PLATE DETAILS

| PARAMETER | DC COMPOUND MOTOR |
|----------------|-------------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

DESCRIPTION:

The characteristics of a compound motor will depend upon whether the series and shunt fields are assisting each other (cumulative) or are opposing each other (differential). In the cumulative connections, the characteristics will be in between those of shunt and series motors whereas for latter, they tend towards those of series motors. Compound motors are used for driving heavy machine tools for intermittent loads, shears, purchasing machines etc.

PRECAUTIONS:

- The motor field rheostat should be kept at minimum resistance position
- At the time of starting the motor should be in no load condition
- The motor should be run in anticlockwise direction

PROCEDURE:


1. Connections are given as per the circuit diagram shown in Fig.
2. Rated voltage is given to the circuit.
3. The field rheostat is adjusted to get the rated speed.
4. Load on the motor is varied and the corresponding voltage, current and speed are noted for different loads on the motor in table.
5. The load is applied until the rated current of the motor is reached.
6. The load is then released and the supply is switched off.
7. Water is applied to the brake drum then and there to avoid heating of the brake drum.

TABULATION


OBSERVATION: Radius of a brake drum= m

| S.No | V _a (volts) | I _L (amps) | I _F (amps) | N(rpm) | Spring Balance | | S ₁ - S ₂ (kg) | Torque N-m | Input (watts) | Output (watts) | Efficiency %η |
|------|---------------------------|--------------------------|--------------------------|--------|----------------|----------------|---|---------------|------------------|-------------------|------------------|
| | | | | | S ₁ | S ₂ | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |


MODEL GRAPH:

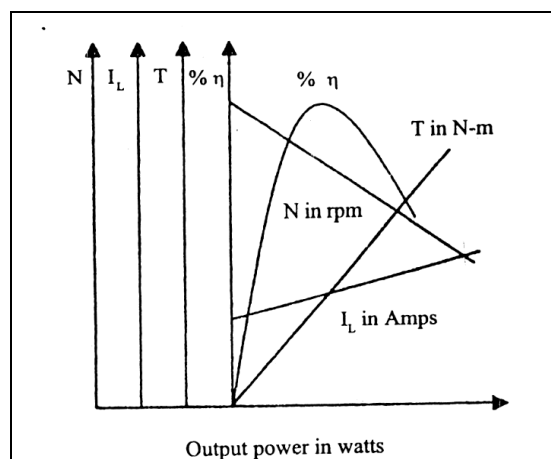

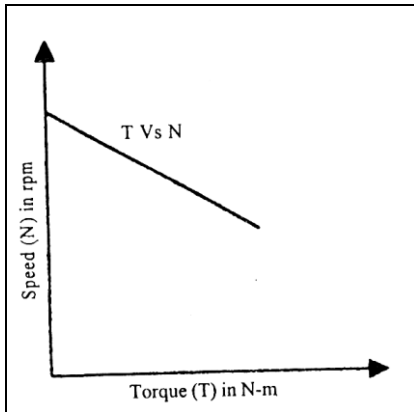Graph Representing the Load Characteristics of DC Compound Motor.



(a). Mechanical Characteristics

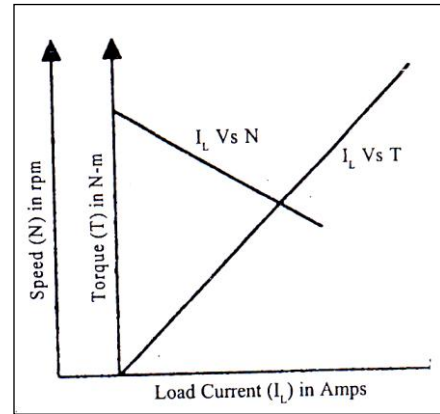

(b). Electrical Characteristics

CALCULATIONS:**RESULT:**

Thus the load test on DC compound motor was conducted and the performance characteristics were drawn.


| | | |
|----------|--|-------------------------------------|
| Ex. No : | | LOAD TEST ON DC SERIES MOTOR |
| Date : | | |

AIM:

To conduct the load test on a given DC series motor and to draw its performance curves.

APPARATUS REQUIRED:

| S.No | Name of the apparatus | Type | Range | Quantity |
|------|-----------------------|------------------|-------------|----------|
| 1 | Ammeter | Moving coil (MC) | (0-20)amps | 1 |
| 2 | Voltmeter | Moving coil (MC) | (0-300)volt | 1 |
| 3 | Tachometer | Digital | - | 1 |
| 4 | Connecting wires | - | - | Required |

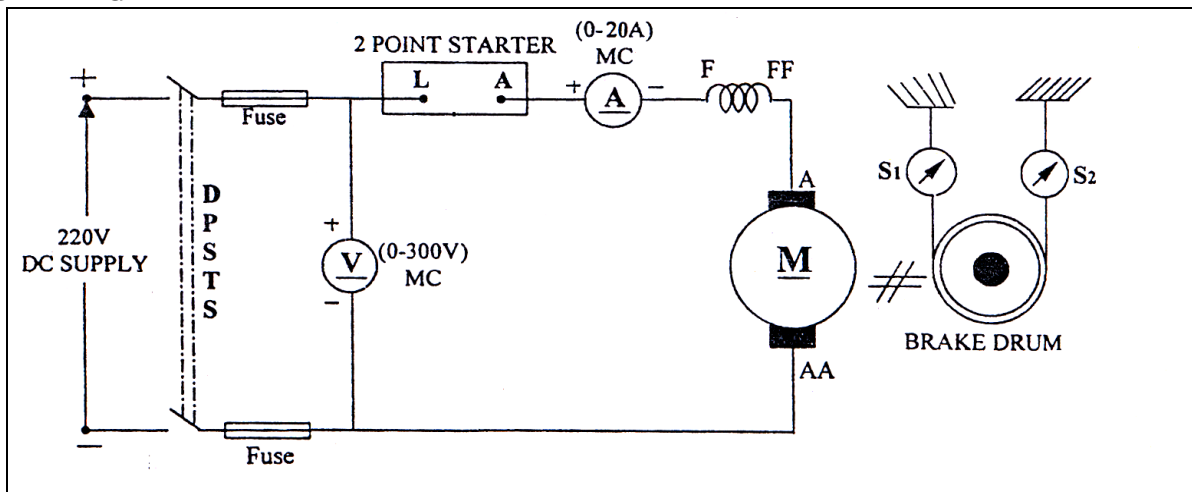CIRCUIT DIAGRAM:**FUSE RATING:**

For Load Test Fuse Rating=125% of rated current.

FORMULA :

$$\text{Torque, } T = (S_1 - S_2) \times \left(R + \frac{t}{2}\right) \times 9.81 \text{ Nm}$$

Where R -radius of brake drum in m

t - thickness of the belt in m

S_1, S_2 -spring balance reading in Kg

$$\text{Input Power, } P_i = V_L I_L \text{ Watts}$$

Where V_L -load voltage in V

I_L -load current in A

$$\text{Output Power, } P_o = \frac{2\pi NT}{60} \text{ Watts}$$

Where N -Speed of the armature in rpm

T -Torque in Nm

$$\% \text{ Efficiency} = \frac{\text{Output Power}}{\text{Input Power}} \times 100$$

NAME PLATE DETAILS

| PARAMETER | DC SERIES MOTOR |
|----------------|-----------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

PRECAUTIONS:

- The motor field rheostat should be kept at minimum resistance position.
- At the time of starting the motor should be in no load condition.
- The motor should be run in anticlockwise direction.

PROCEDURE:


1. Connections are given as per the circuit diagram
2. Initially apply some load.
3. Using the two point starter the motor is started to run
4. The meter readings are noted
5. By using the break drum with spring balance arrangement the motor is loaded and the corresponding readings are noted up-to the rated current
6. After the observation of all the readings the load is released gradually not fully
7. The motor is switched off.

TABULATION


OBSERVATION: Radius of a brake drum=-----m

| S.No | V _a (volts) | I _L (amps) | I _F (amps) | N (rpm) | Spring Balance | | S ₁ - S ₂ (kg) | Torque (N-m) | Input (watts) | Output(watts) | Efficiency %η |
|------|---------------------------|--------------------------|--------------------------|------------|----------------|----------------|---|-----------------|------------------|-------------------|------------------|
| | | | | | S ₁ | S ₂ | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |
| | | | | | | | | | | | |


MODEL GRAPH:

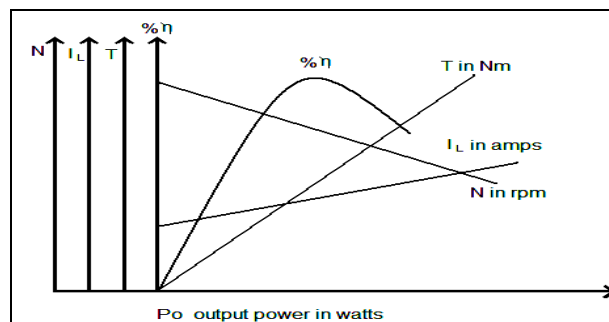

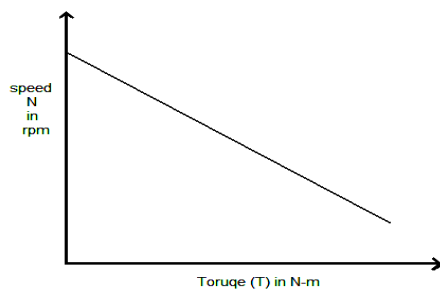Graph representing the load characteristics of dc series motor.



Mechanical Characteristics

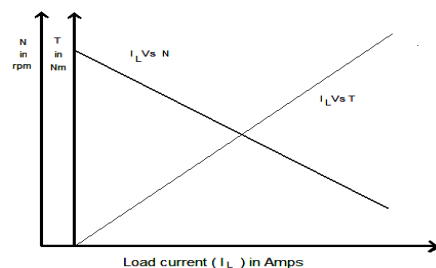

Electrical Characteristics

CALCULATIONS:

RESULT:

Thus the load test on dc series motor was conducted and the performance curves were drawn.

VIVA QUESTIONS:

1. Why the DC series motor should not operate without load?
2. Can A DC Series Motor operate on Ac Supply?
3. Why DC Series motor is called as Variable speed motor?
4. What are the applications of dc series motor?
5. Why is DC series motor not suitable for belt driven loads?


| | | |
|----------|--|-------------------------|
| Ex. No : | | SWINBURNE'S TEST |
| Date : | | |

AIM:

To predetermine the efficiency of a given DC shunt machine by Swinburne's test and to draw the characteristics curves.

APPARATUS REQUIRED:

| S.No | Name of the Apparatus | Type | Range | Quantity |
|------|-----------------------|-----------------|---|----------|
| 1. | Ammeter | Moving coil(MC) | (0-2)amps, (0-5)amps | Each 1 |
| 2. | Ammeter | Moving coil(MC) | (0-10)amps | 1 |
| 3. | Voltmeter | Moving coil(MC) | (0-300)volts,(0-10)volts | Each 1 |
| 4. | Rheostat | Wire Wound | 300 Ω /2amps, 50 Ω /5amps | Each 1 |
| 5. | Tachometer | Digital | - | 1 |
| 6. | Connecting wires | - | - | Required |

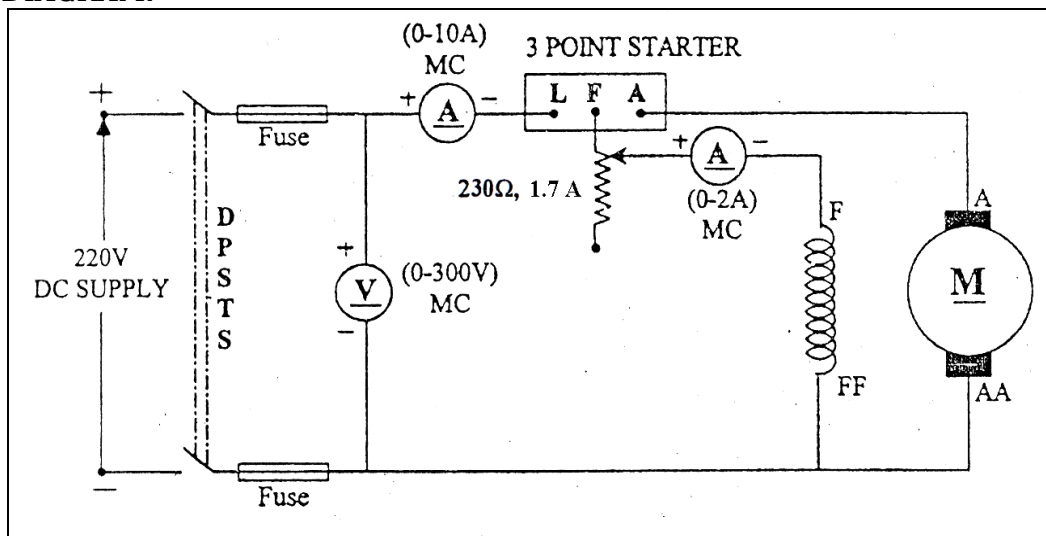CIRCUIT DIAGRAM:


The Circuit Diagram for Swinburne's Test

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | DC SHUNT MOTOR |
|----------------|----------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

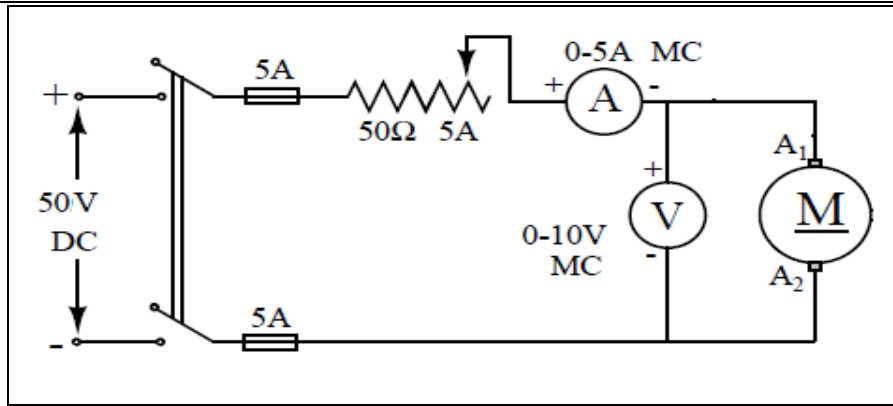

Circuit Diagram to find the Armature Resistance.

FORMULAE:

1. Armature Resistance (R_a) = $1.6 \times R_{dc}$ in Ohm.

Where 1.6 Adds the Skin Effect

R_{dc} = Resistance Of The Armature Coil When It Is Energized

By DC Supply

2. Constant Loss (W_{co}) = $(V_{I_0} - I_{a_0}^2 R_a)$ in W

Where V = Terminal Voltage in V

I_0 = No Load Current in A

I_{a_0} = No Load Armature Current In A.

3. Armature Current (I_a) = $(I_l + I_f)$ In A.

Where +ve is Used For Generator

- ve is Used For Motor.

4. Copper Loss (W_{Cu}) = $I_a^2 R_a$ in W.

5. Total Loss (W_{total}) = Constant Loss + Copper Loss in W.

6. Input Power for Motor (W_i)/Output Power for Generator (W_o) = W_i/W_o W

7. Output Power For Motor (W_o) = (Input Power - Total Losses) in W

8. Input Power For Generator (W_i) = (Output Power + Total Losses) in W.

9. Percentage of Efficiency = $(\text{Output Power} / \text{Input Power}) \times 100$

DESCRIPTION:

Swinburne's test is also called no load or losses method. It is the simplest indirect method where losses are measured separately and then the efficiency is predetermined at any desired load conditions. This method is economical since power required to test a large machine is very small and no cooling circuit is required as in load test. This method is not suitable for DC series motor as it cannot be operated under no load condition.

PRECAUTIONS:

- The Motor Field Rheostat Should Be Kept At Minimum Resistance Position.
- The Motor Should Be At No Load Condition Throughout The Experiment.

PROCEDURE:

1. Connections are given as per the circuit diagram shown in Fig.
2. By using the three point starter the motor is started to run at the rated speed.
3. The meter readings are noted at no load condition.
4. The motor is switched off using the DPST switch.
5. After that the armature resistance test is conducted as per the circuit diagram and the voltage and current are noted for various resistive loads.
6. After the observation of readings the load is released gradually.

TABULATION:

| S.No | Terminal Voltage (volts) | No Load Current (amps) | Field Current (amps) | No Load Armature Current (I_{a0}) (amps) | Constant Loss (watts) |
|------|--------------------------|------------------------|----------------------|--|-----------------------|
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |

TABULATION TO FIND ARMATURE RESISTANCE:

| S.No | Armature Current (I_a) (amps) | Armature Voltage (V_a) (volts) | Armature Resistance $R_a = V_a / I_a$ (Ohms) |
|------|-----------------------------------|------------------------------------|--|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

RESULTANT TABULATION TO FIND OUT THE EFFICIENCY OF THE MACHINE WHEN RUNNING AS MOTOR/GENERATOR


Armature Resistance (R_a) = ohm Rated Current (I_r) = amps
 Constant Loss (W_{co}) = watts Field Current (I_f) = amps
 Terminal Voltage (V) = volts

RUNNING AS A MOTOR

| S.NO | Fraction of load (X) | Load current $I_L = X I_r$ (amps) | Armature current $I_a = I_L I_r$ (watts) | Armature cu loss $W_{cu} = I_a^2 R_a$ (watts) | Total loss W_{Total} (watts) | Input power $W_i = V I_L$ (watts) | Output power $W_o = W_i - W_{Total}$ (watts) | Efficiency $\eta = W_o / W_i$ % |
|------|----------------------|-----------------------------------|--|---|--------------------------------|-----------------------------------|--|---------------------------------|
| 1 | 1/4 | | | | | | | |
| 2 | 1/2 | | | | | | | |
| 3 | 3/4 | | | | | | | |
| 4 | 1 | | | | | | | |

RUNNING AS A GENERATOR

| S.NO | Fraction of load (X) | Load current $I_L = X I_r$ (amps) | Armature current $I_a = I_L I_r$ (watts) | Armature cu loss $W_{cu} = I_a^2 R_a$ (watts) | Total loss W_{Total} (watts) | Input power $W_i = V I_L$ (watts) | Output power $W_o = W_i - W_{Total}$ (watts) | Efficiency $\eta = W_o / W_i$ % |
|------|----------------------|-----------------------------------|--|---|--------------------------------|-----------------------------------|--|---------------------------------|
| 1 | 1/4 | | | | | | | |
| 2 | 1/2 | | | | | | | |
| 3 | 3/4 | | | | | | | |
| 4 | 1 | | | | | | | |

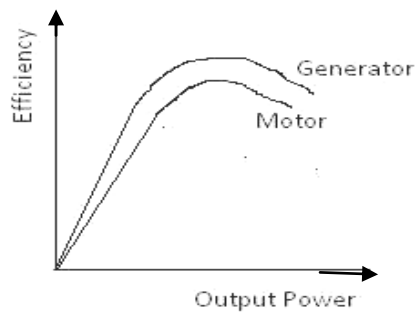MODEL GRAPH:

Performance Characteristics

CALCULATIONS:**RESULT:**

Thus the efficiency of a given DC shunt machine is calculated by conducting Swinburne's test.

VIVA QUESTIONS:

1. In which type of dc machine, Swinburne's test is applicable?
2. What are the advantages of Swinburne's test?
3. What are the causes of overheating of a dc motor?
4. Why is shaft torque less than armature torque in a dc motor?
5. What is the necessity of a starter in a dc motor?

Ex. No :

Date :


SPEED CONTROL OF DC SHUNT MOTOR

AIM:

To conduct an experiment to control the speeds of the given DC shunt motor by field and armature control method and to draw its characteristic curves.

APPARATUS REQUIRED:

| S.No | Name of the apparatus | Type | Range | Quantity |
|------|-----------------------|-----------------|--------------------------|----------|
| 1. | Ammeter | Moving coil(MC) | (0-2)amps | 1 |
| 2. | Ammeter | Moving coil(MC) | (0-5)amps | 1 |
| 3. | Voltmeter | Moving coil(MC) | (0-300)volts | 1 |
| 4. | Rheostat | Wire wound | (230 Ω ,1.7 amps) | 1 |
| 5. | Rheostat | Wire wound | (50 Ω ,5amps) | 1 |
| 6. | Tachometer | Digital | - | 1 |
| 7. | Connecting wires | - | - | Req |

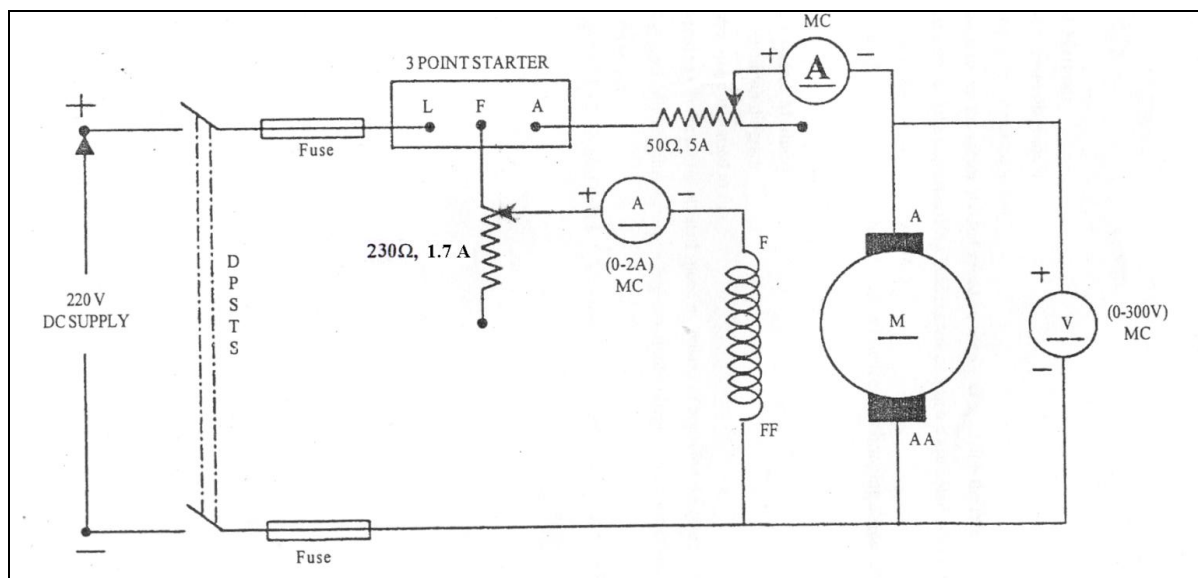CIRCUIT DIAGRAM:**FUSE RATING:**

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | DC SHUNT MOTOR |
|----------------|----------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

PRECAUTIONS:

- The motor field rheostat should be kept at minimum resistance position.
- The motor armature rheostat should be kept at maximum resistance position.
- The motor should be in no load condition throughout the experiment.
- The motor should be run in anticlockwise direction.

PROCEDURE:**FIELD CONTROL METHOD (FLUX CONTROL METHOD)**


1. Connections are given as per circuit diagram.
2. Using the three point starter the motor is started to run.
3. The armature rheostat is adjusted to run the motor at rated speed by means of applying the rated voltage.
4. The field rheostat is varied gradually and the corresponding field current and speed are noted up to 120% of the rated speed by keeping the armature current as constant.
5. The motor is switched off using the DPST switch after bringing all the rheostats to their initial position.

ARMATURE CONTROL METHOD (VOLTAGE CONTROL METHOD)


1. Connections are given as per circuit diagram
2. Using the three point starter the motor is started to run.
3. The armature rheostat is adjusted to run the motor at rated speed by means of applying the rated voltage.
4. The armature rheostat is varied gradually and the corresponding armature voltage and speed are noted up to the rated voltage.
5. The motor is switched off using the DPST (Double pole single throw) switch after bringing all the rheostats to their initial position.

TABULATION FOR SPEED CONTROL OF DC SHUNT MOTOR

| S.NO | Armature Control Method | | Field Control Method | |
|------|----------------------------------|---------------|------------------------------|---------------|
| | Field Current (I_f) = | | Armature Voltage (V_a) = | |
| | Armature Voltage (V_a) volts | Speed (N) Rpm | Field Current (I_f) amps | Speed (N) Rpm |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

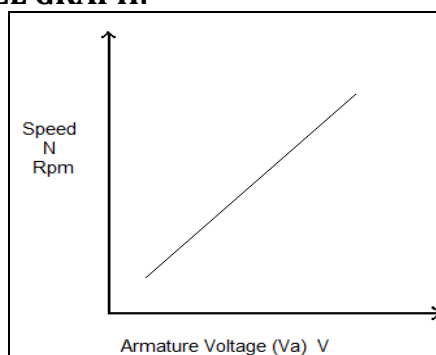MODEL GRAPH:

Armature Control Method

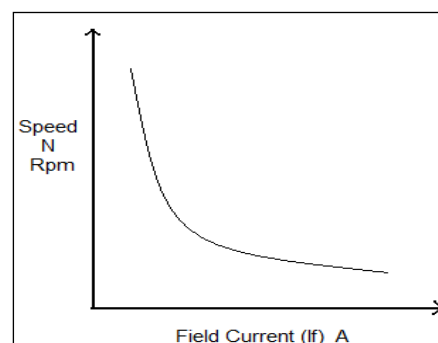

Field Control Method

RESULT:

Thus the speed of the DC shunt motor is controlled by conducting field control and armature control method.

VIVA QUESTIONS:

1. Why is the speed of a shunt motor practically constant?
2. What will happen if a shunt motor running at no load has its shunt winding opened accidentally?
3. When will you say the motor is running at base speed?
4. Why a dc shunt motor is found suitable to drive fans?
5. What happens when the load is increased in shunt motor?

| | | |
|----------|--|---|
| Ex. No : | | HOPKINSON'S TEST ON DC MOTOR - GENERATOR SET |
| Date : | | |

AIM:

To Perform Hopkinson's Test on two identical DC machine and to predetermine the efficiency of the motor and generator at 25%,50%,75%,100% and 125% of rated current.

APPARATUS REQUIRED:

| S.No | Name of the Equipment | Type | Range | Quantity |
|------|-----------------------|------------------|-----------------------------|-------------|
| 1 | Rheostat | Wire wound | 230Ω/1.7amps, 300Ω/2amps | Each 1 |
| 2 | Voltmeter | Moving colis(MC) | (0-300)volts | 2 |
| 3 | Ammeter | Moving colis(MC) | (0-2)amps | 1 |
| 4. | Ammeter | Moving colis(MC) | 0-20)amps | 2 |
| 5. | Connecting wires | - | | As required |

FORMULAE:

1. Armature copper loss in generator = $I_a^2 R_a$ in ohms

2. Armature copper loss in motor = $(I_1 + I_2)^2 R_a$ in ohms

3. Total power drawn from the supply = $V I_1$ in watts

Let the sum of iron losses and mechanical losses of each machine be then

4. $V I_1 = 2 W_C + I_a^2 R_a + (I_1 + I_2)^2 R_a$ watts

5. $W_C = 1/2 [2 W_C + I_a^2 R_a + (I_1 + I_2)^2 R_a]$ watts

Efficiency of motor:

1. Shunt field copper loss of motor = $V I_3$ watts

2. Total losses of motor = $W_C + (I_1 + I_2)^2 R_a + V I_3$ watts

3. Power output to motor (P_{IM}) = armature input + shunt field input
 $= V(I_1 + I_2) + V I_3$ watts

4. Motor losses (W) = Armature cu loss + shunt field cu loss + stray losses
 $= W_C + (I_1 + I_2)^2 R_m + V I_3$ watts

5. $\% \eta = P_{IM} - W_M / P_{IM} * 100$

Efficiency of generator:

1. Generator output (P_{go}) = $V I_2$ watts

2. Generator losses (W_g) = armature cu loss + shunt field cu loss + stray loss
 $= W_C + I_2^2 R_a + V I_4$ watts

3. $\% \eta = P_{go} / P_{go} + W_g * 100$

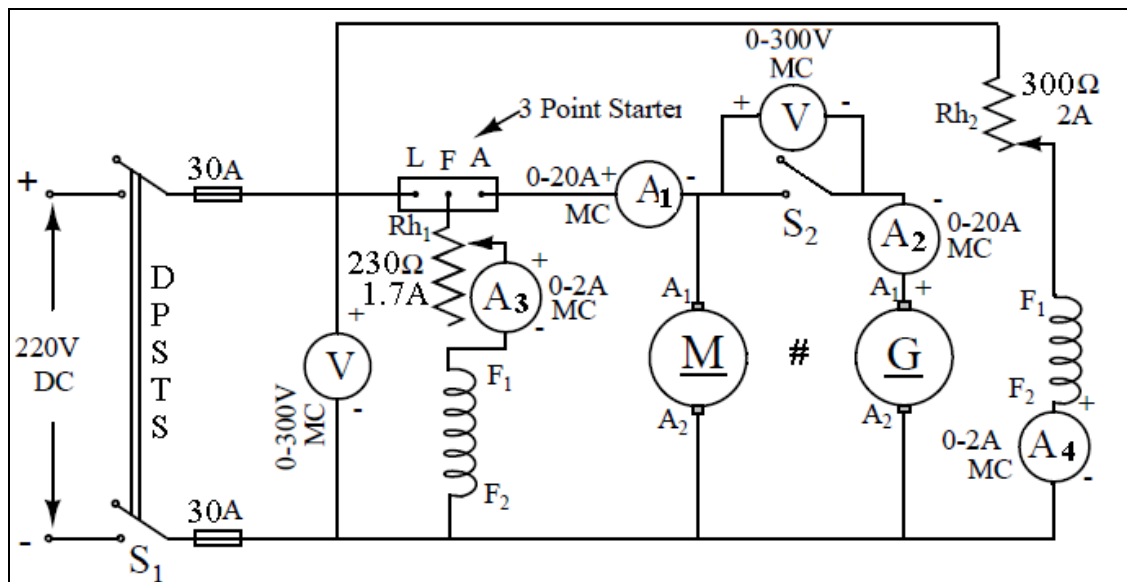
CIRCUIT DIAGRAM:

Fig. Circuit Diagram For Hopkinson's Test

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | DC SHUNT MOTOR |
|----------------|----------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

DESCRIPTION:

It is also called regenerative or back-to-back test. For this test two identical machines are used. The two machines are mechanically coupled and are so adjusted electrically that one of them act as motor and another as generator. The mechanical output of the motor drives the generator and the electrical output of the generator is used in supplying the greater part of the input to the motor in addition to the power drawn from the supply mains. The machine with small excitation acts as motor and with large excitation acts as generator. Since the machines can be tested under full load conditions for long duration, the performance of the machines regarding commutation and temperature rise can be studied.

PRECAUTIONS:

- Motor Field rheostat should be in minimum resistance position and generator Field rheostat should be in maximum resistance position at the time of starting.
- The SPDT switch is closed when the machines are exactly out of phase (i.e.) the voltmeter should indicate zero.


PROCEDURE:

1. Note the name plate details and justify the range of meters selected.
2. Make the connections as per the circuit diagram.
3. Keep the SPST switch open, give the supply to the motor and start it with the help of three point starters.
4. Adjust the field of the motor to the rated value by varying the rheostat provided in the motor field circuit.
5. Adjust the rheostat in the field circuit of generator, so that the generated voltage of the generator is equal to the supply voltage.

6. Check the voltage across adjust the switch S. In case of wrong polarity the voltmeter across the switch 'S' will record twice the supply voltage. In such a case, switch off the mains and reverse the armature terminals of the generator. Repeat steps 3,4 & 5. Now the voltmeter will indicate zero voltage. Close the switch 'S' after ensuring that the voltmeter reads zero. Under this condition, the machine working as a generator is just floating (i.e) neither drawing any current from nor giving into the lines.

TABULATION:

| S.No | Voltage (V) (volts) | Current(I ₁) (amps) | Current(I ₂) (amps) | Current(I ₃) (amps) | Current(I ₄) (amps) |
|------|------------------------|------------------------------------|------------------------------------|------------------------------------|------------------------------------|
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |

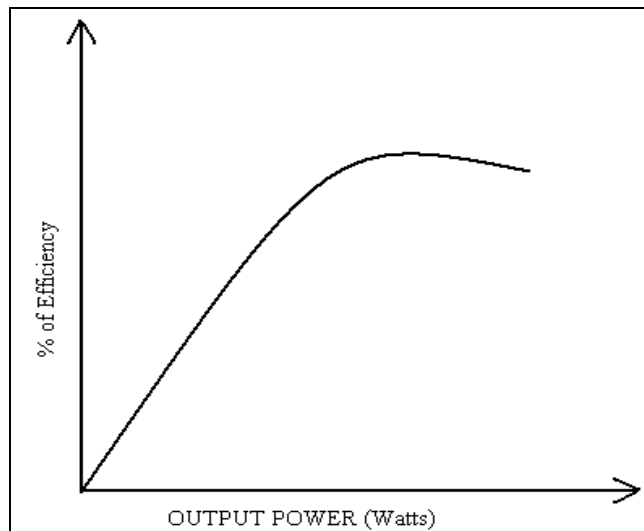MODEL GRAPH:

Model Graph For Hopkinson's Test

CALCULATIONS:

RESULT:

Thus the Hopkinson's test was conducted on two identical DC machines and their efficiencies were predetermined.

VIVA QUESTIONS:

1. How may the number of parallel paths in an armature be increased?
2. How are brushes connected in a DC generator?
3. What is the best way of minimizing eddy currents in an armature?
4. How should the armature be laminated for purpose?
5. What causes sparking at the brushes?

Ex. No :

Date :

LOAD TEST ON SINGLE PHASE TRANSFORMER


AIM:

To conduct the load test on a given single phase transformer and to draw its performance curves.

APPARATUS REQUIRED:

| S.No | Name of The Apparatus | Type | Range | Quantity |
|------|-----------------------|-----------------------|--------------------|----------|
| 1 | Ammeter | Moving Iron(MI) | (0-10) amps | 2 |
| 2 | Voltmeter | Moving Iron(MI) | (0-300) volts | 2 |
| 3 | Wattmeter | Unity power factorUPF | (300volts, 10amps) | 2 |
| 4 | Resistive Load | - | 2 kilo watts(kW) | 1 |
| 5 | Connecting wires | - | - | Required |

CIRCUIT DIAGRAM:

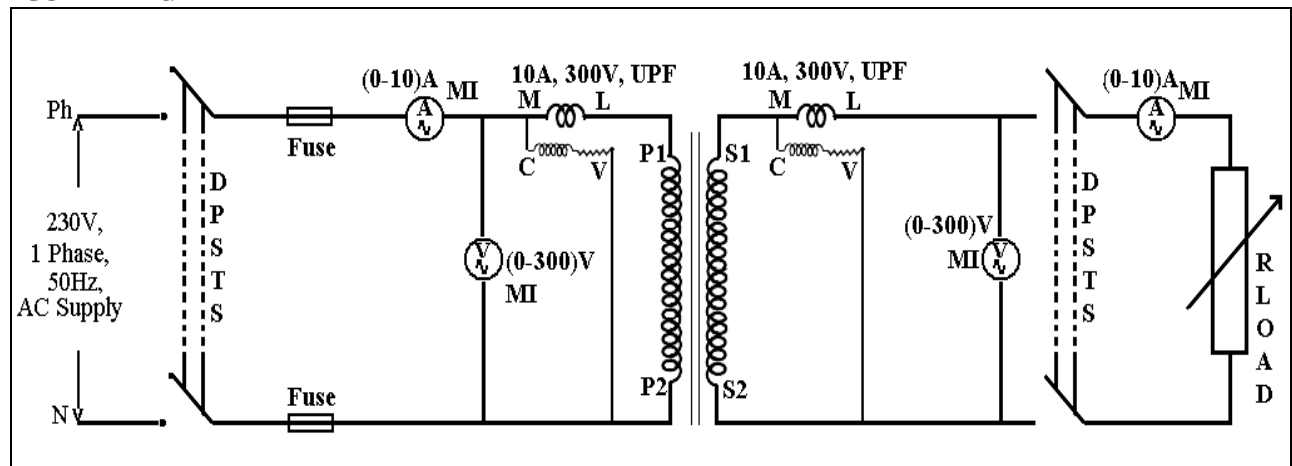

NAME PLATE DETAILS

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

| PARAMETER | TRANSFORMER | |
|----------------|-------------|-----------|
| | Primary | Secondary |
| Rating(kw) | | |
| Voltage(volts) | | |
| Current(amps) | | |

FORMULAE:

$Input\ Power = (Wattmeter\ reading \times Multiplication\ Factor)$ in W Where,

$$Multiplication\ Factor = \frac{(Rating\ of\ Pressure\ coil \times Rating\ of\ current\ Coil \times Power\ Factor)}{Full\ scale\ Reading}$$

$Output\ Power = V_{sec} \times I_{sec} \times \cos\phi$ in W

$$\% Efficiency = \frac{Output\ Power}{Input\ Power} \times 100$$

$$\% Regulation = \frac{V_{NL} - V_{LOAD}}{V_{NL}} \times 100$$

V_{NL} = No load voltage in volts.

V_{LOAD} = Load voltage in volts.


PRECAUTIONS:

- At the time of starting transformer should be at no load condition.
- High voltage and low voltage sides of the transformer should be properly used as primary or secondary respective experiments.

PROCEDURE:

1. The circuit diagram for load test on single-phase transformer is shown in fig
2. Connections are given as per the circuit diagram.
3. The DPST Switch on the primary side is closed and the DPST Switch on the Secondary side is opened.
4. The Autotransformer is adjusted to energize the transformer with rated primary voltage.
5. The Voltmeter and Ammeter readings are noted and tabulated at no load condition.
6. The DPST switch on the secondary side is closed.
7. The transformer is loaded up to 130% of the Rated load, corresponding Ammeter, Voltmeter and Wattmeter readings are noted and tabulated.
8. After the observation of all the readings the load is released gradually to its initial position.
9. The Autotransformer is brought to its initial position.
10. The Supply is switched off.

MODEL GRAPH:

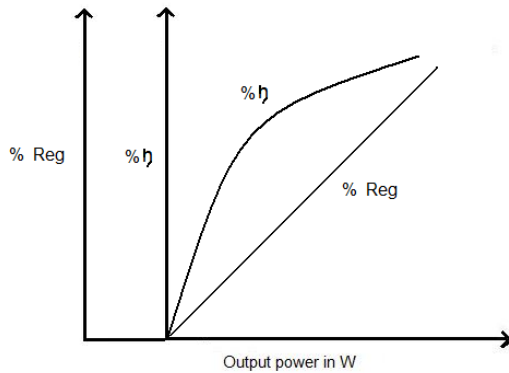

TABULATION FOR LOAD TEST OF SINGLE PHASE TRANSFORMER

| S.No | Pri. Voltage (V _{pri}) volts | Pri. Current (I _{pri}) amps | Sec. Voltage (V _{sec}) volts | Sec. Current (I _{sec}) amps | Input Wattmeter readings (watts) | | Output Wattmeter readings (watts) | | Input Power watts | Output Power watts | % η | %Reg |
|------|--|---------------------------------------|--|---------------------------------------|----------------------------------|-----|-----------------------------------|-----|-------------------|--------------------|-----|------|
| | | | | | Obs | Act | Obs | Act | | | | |
| | | | | | | | | | | | | |
| | | | | | | | | | | | | |
| | | | | | | | | | | | | |
| | | | | | | | | | | | | |
| | | | | | | | | | | | | |

CALCULATIONS:**RESULT:**

Thus the load test on single-phase transformer was conducted and performance characteristics curves were drawn.

VIVA QUESTIONS:

1. What is a transformer?
2. What is the principle of operation of transformer?
3. What is transformation ratio?
4. What is an ideal transformer?
5. How will you relate the EMF induced in the transformer with the frequency of the applied voltage?

Ex. No :


Date :

LOAD TEST ON THREE PHASE TRANSFORMER**AIM:**

To conduct the load test on a given three phase transformer and to determine its efficiency and regulation.

APPARATUS REQUIRED:

| S.No | Name of The Apparatus | Type | Range | Quantity |
|------|-----------------------|--|----------------------------------|----------|
| 1 | Voltmeter | Moving Iron(MI) | 0-600 volts | 1 |
| 2 | Voltmeter | Moving Iron(MI) | 0-300 volts | 1 |
| 3 | Ammeter | Moving Iron(MI) | 0-10 amps | 1 |
| 4 | Ammeter | Moving Iron(MI) | 0-20amps | 1 |
| 5 | Wattmeter | Unity poer factor(UPF), Double element | 600volts/10amps, 300volts/20amps | Each 1 |
| 6 | Resistive load | Wire Wound | 3ph 415volts,5kW | 1 |
| 7 | Transformer | Inductive | 3ph 440/220volts | 1 |
| 8 | Connecting wires | - | - | Required |

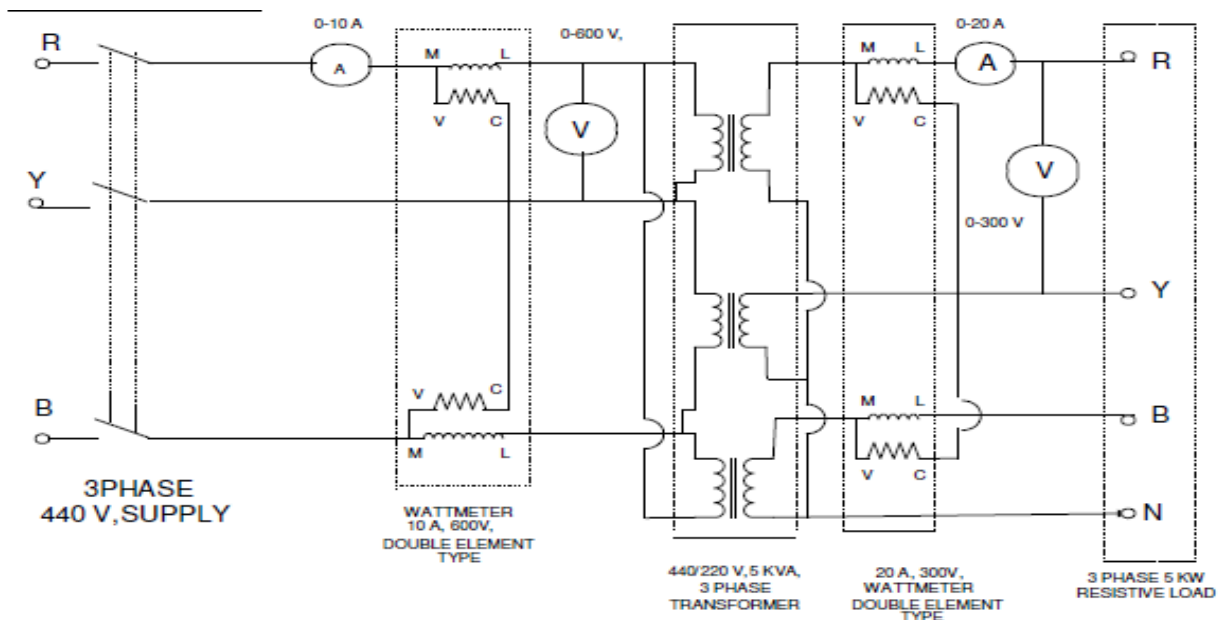CIRCUIT DIAGRAM:**FUSE RATING:**

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | TRANSFORMER | |
|----------------|-------------|----|
| | Py | Sy |
| Rating(kw) | | |
| Voltage(volts) | | |
| Current(amps) | | |

PRECAUTIONS:

All the switches should be kept open.

The auto transformer should be kept at minimum potential position.

PROCEDURE:

- 1) Connect the circuit as shown in figure.
- 2) Keep load on transformer at off position.
- 3) Keeping dimmer stat at zero position, switch on 3-Phase supply.
- 4) Now increase dimmer stat voltage for 440 volts.
- 5) Note down the no-load readings.
- 6) Then increase the load in steps till rated current of the transformer & note down corresponding readings.
- 7) Calculate efficiency & regulation for each reading.

FORMULAE:

Input power = $W_1 + W_2$ Watts

Output power = $\sqrt{3} V_2 I_2$ Watts

%Efficiency = (output / Input) x 100

%Regulation = $(V_{NL} - V_L) / V_L$

TABULATION FOR LOAD TEST OF THREE PHASE TRANSFORMER

| S.No | V ₁ Volts | I ₁ Amps | M.F = | | V ₂ Volts | I ₂ Amps | M.F = | | Efficiency | Regulation |
|------|-------------------------|------------------------|-------------------------|-----|-------------------------|------------------------|-------------------------|-----|------------|------------|
| | | | W ₁ Watts | | | | W ₂ Watts | | | |
| | | | OBS | ACT | | | OBS | ACT | | |
| | | | | | | | | | | |
| | | | | | | | | | | |
| | | | | | | | | | | |
| | | | | | | | | | | |
| | | | | | | | | | | |

CALCULATIONS:**RESULT:**

Thus the load test on three phase transformer was conducted and its efficiency and regulation were determined.


| | | |
|----------|--|---|
| Ex. No : | | OPEN CIRCUIT TEST AND SHORT CIRCUIT TEST ON SINGLE PHASE TRANSFORMER |
| Date : | | |

AIM:

To predetermine the efficiency and regulation of a given single Phase transformer by conducting the open circuit test and short circuit test also to draw its Equivalent circuit.

APPARATUS REQUIRED:

| S. No | Name of the apparatus | Type | Range | Quantity |
|-------|-----------------------|-----------------------|---------------------------|----------|
| 1 | Ammeter | Moving Iron(MI) | (0-2) amps | 1 |
| 2 | Ammeter | Moving Iron(MI) | (0-10)amps, (0-20)amps | Each 1 |
| 4 | Voltmeter | Moving Iron(MI) | (0-150)volt | 1 |
| 5 | Voltmeter | Moving Iron(MI) | (0-300)volt | 1 |
| 6 | Voltmeter | Moving Iron(MI) | (0-75)volt | 1 |
| 7 | Wattmeter | Low power factorLPF | (150volts,1amp) | 1 |
| 8 | Wattmeter | Unity power factorUPF | (150volts,10amps) | 1 |
| 9 | Auto transformer | 1Phase | 230/(0-270) volt | 1 |
| 10 | Transformer | 1Phase | 1kVA,(115/230)volt | 1 |
| 11 | Connecting wires | - | - | Required |

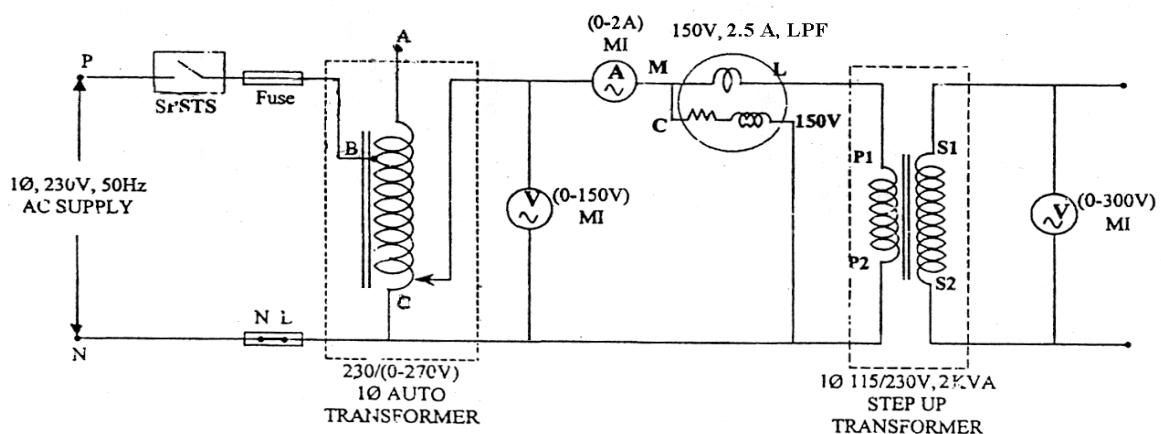
CIRCUIT DIAGRAM**Open circuit test:****FUSE RATING:**

For No Load Test Fuse Rating=10% of rated current.

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | TRANSFORMER | |
|----------------|-------------|----|
| | Py | Sy |
| Rating(kw) | | |
| Voltage(volts) | | |
| Current(amps) | | |

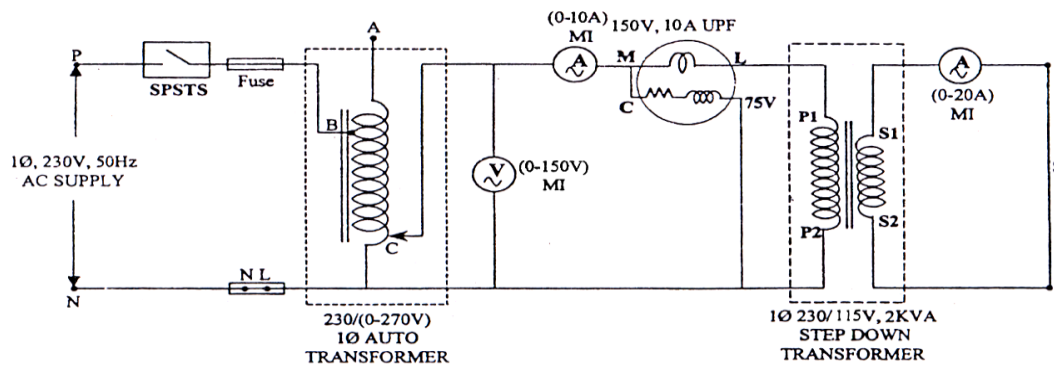Short circuit test:**FORMULAE:****OPEN CIRCUIT TEST:**

$$\text{No load power factor } (\cos \phi_0) = \frac{W_{oc}}{V_{oc} I_{oc}} \quad W$$

Where, W_{oc} - open circuit power in watts

V_{oc} - open circuit voltage in volts

I_{oc} - open circuit current in amps

$$\text{No load working component Resistance } (R_0) = \frac{V_{oc}}{I_{oc} \times \cos \phi} \quad \Omega$$

$$\text{No load magnetising component reactance } (X_0) = \frac{V_{oc}}{I_{oc} \times \sin \phi} \quad \Omega$$

SHORT CIRCUIT TEST:

$$\text{Equivalent impedance referred to Hv side } (Z_{02}) = \frac{V_{sc}}{I_{sc}} \quad \Omega$$

Where, V_{sc} - short circuit voltage in volts

I_{sc} - short circuit current in amps

$$\text{Equivalent resistance referred to Hv side } (R_{02}) = \frac{W_{sc}}{I_{sc}^2} \quad \Omega$$

Where, W_{sc} - short circuit power in watts

$$\text{Equivalent reactance referred to Hv side } (X_{02}) = (Z_{02}^2 - R_{02}^2) \quad \Omega$$

$$\text{Transformer ratio } (K) = \frac{V_2}{V_1}$$

Where, V_1 = Primary voltage in volts

V_2 = Secondary voltage in volts

$$\text{Equivalent resistance referred to Lv side } (R_{01}) = \frac{R_{02}}{K^2} \quad \Omega$$

$$\text{Equivalent reactance referred to Lv side } (X_{01}) = \frac{X_{02}}{K^2} \quad \Omega$$

TO DETERMINE THE EFFICIENCY AND REGULATION:

$$\text{Output Power} = (X \times KVA \times \cos \phi) \quad W$$

Where, X = Fraction of load

KVA = Power Rating of Transformer

$\cos \phi$ = power factor

$$\text{Copper loss} = (X_2 \times W_{sc}) \quad W$$

Where, W_{sc} - copper loss in short circuit condition

$$\text{Total loss} = (\text{Copper loss} + \text{Iron loss}) \quad W$$

$$\% \eta = \frac{\text{Output power}}{(\text{Output Power} + \text{Losses})} \times 100$$

$$\% \text{ Regulation} = X \times I_{sc} \frac{[R_{02} \times \cos \phi + X_{02} \times \sin \phi]}{V_{oc}} \times 100$$

where, + for lagging & - for leading

PRECAUTIONS:

- At the time of starting transformer should be at no load condition.
- High voltage and low voltage sides of the transformer should be properly used a primary secondary respective for the experiments.

PROCEDURE:

OPEN CIRCUIT TEST:

1. Connections are made as per the circuit diagram.
2. The Double Pole Single Throw (DPST) Switch on the primary side is closed.
3. The autotransformer is adjusted to energize the transformer with rated voltage on the low voltage(LV) side.
4. The voltmeter, Wattmeter and Ammeter Readings are noted at no load condition.
5. The auto transformer is brought to its initial position.
6. The supply is switched off.

SHORT CIRCUIT TEST:

1. Connections are made as per the circuit diagram
2. The DPST Switch on the primary side is closed
3. The autotransformer is adjusted to energize the transformer with rated current on the high voltage(HV) side.
4. The voltmeter, Wattmeter and Ammeter Readings are noted at short circuit condition
5. The auto transformer is brought to its initial position and switch off the power supply.

TABULATION FOR OPEN CIRCUIT TEST:

Multiplication Factor =

| S.No | Open Circuit Primary Current (I_{oc}) amps | Open Circuit Primary Voltage (V_{oc}) volts | Open Circuit Power (W_{oc}) watts | | Open Circuit Secondary Voltage (V_{2s}) volts |
|------|--|---|---------------------------------------|-----|---|
| | | | Obs | Act | |
| | | | | | |

TABULATION FOR SHORT CIRCUIT TEST

Multiplication Factor =

| S.No | Short Circuit Primary Current (I_{sc}) amps | Short Circuit Primary Voltage (V_{sc}) volts | Short Circuit Power (W_{sc}) watts | | Short Circuit Secondary Current (I_{2o}) amps |
|------|---|--|--|-----|---|
| | | | Obs | Act | |
| | | | | | |

RESULTANT TABULATION TO FIND OUT THE EFFICIENCY

Core (or) Iron loss (W_i) =


kVA Rating of Transformer =

Rated Short Circuit Current (I_{sc}) =


Short Circuit Power (W_{sc}) =

| Fraction of Load (X) | Short circuit current (I_{sc}) | Output Power = X x kVA x Cos ϕ in watts | | | | | Copper Loss ($X^2 \times W_{sc}$) | Total Loss $W_T = W_i + W_{sc}$ | % η |
|----------------------|------------------------------------|--|-----|-----|-----|---|-------------------------------------|---------------------------------|----------|
| | | 0.2 | 0.4 | 0.6 | 0.8 | 1 | | | |
| 1/4 | | | | | | | | | |
| 1/2 | | | | | | | | | |
| 3/4 | | | | | | | | | |
| 1 | | | | | | | | | |


MODEL GRAPH:

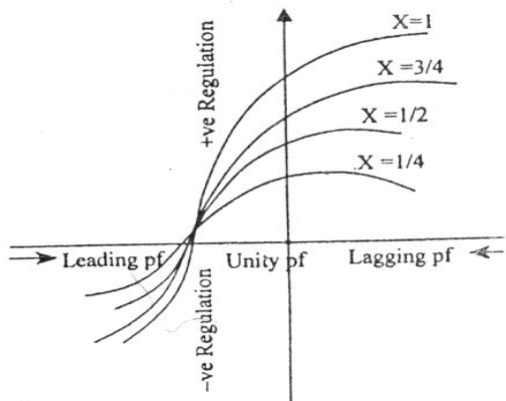

Output power vs Regulation

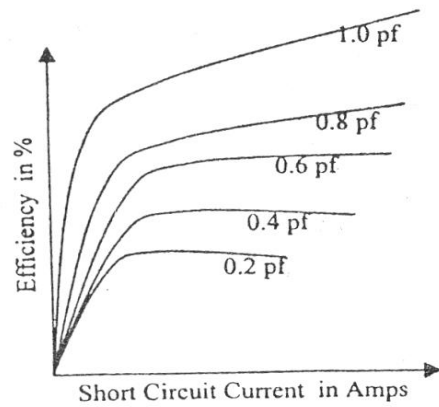

Efficiency vs Short circuit Current

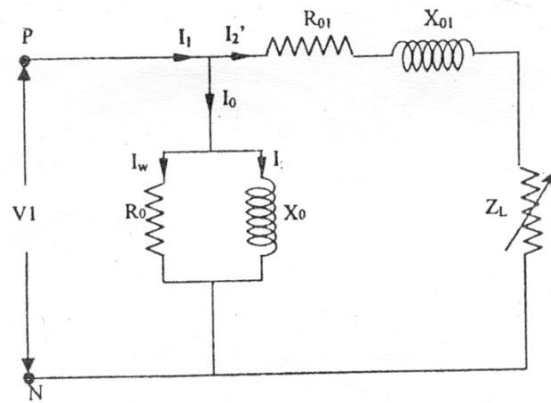

Equivalent circuit of single phase transformer

CALCULATIONS:

RESULT:

Thus the efficiency and regulation of a single phase transformer was calculated by conducting the open circuit and short circuit test and the equivalent circuit was drawn.

VIVA QUESTIONS:

1. Give the condition for maximum efficiency of the transformer.
2. What do you mean by voltage regulation of a transformer?
3. Why the rating of transformer is in kVA?
4. What is all day efficiency?
5. How will you reduce the eddy current loss in the core?

Ex. No :

Date :

POLARITY TEST ON SINGLE PHASE TRANSFORMER**AIM:**


To determine the polarity of a single phase transformer.

APPARATUS REQUIRED:

| S.NO. | APPARATUS REQUIRED | TYPE | RANGE | QUANTITY |
|-------|--------------------|-----------------|------------------------|----------|
| 1 | Voltmeter | Moving Iron(MI) | (0-300)volts | 3 |
| 2 | Auto Transformer | 1Phase | 230/(0-270)volts | 1 |
| 3 | Transformer | 1Phase | 1kVA (230/230)volts | 1 |
| 4 | Connecting wires | - | - | Req |

THEORY:

It is essential to know the relative polarity at any instant of primary and secondary terminals for making correct connections. When the two transformers are to be connected in parallel to share the load on the system. The marking is correct if voltage V_3 is less than V_1 , such a polarity is termed as subtractive polarity. The standard practice is to have subtractive polarity because it reduces the voltage stress between adjacent loads. In case $V_3 > V_1$, the emf induced in primary and secondary have additive relation and transformer is said to have additive polarity.

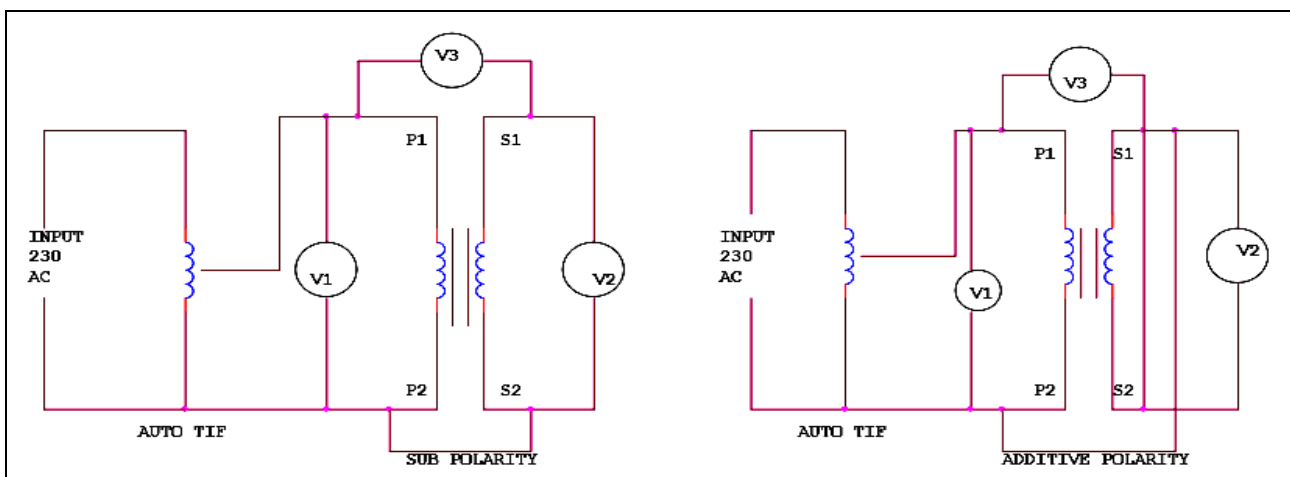CIRCUIT DIAGRAM:**FUSE RATING:**

For No Load Test Fuse Rating=10% of rated current.

NAME PLATE DETAILS

| PARAMETER | TRANSFORMER | |
|----------------|-------------|----|
| | Py | Sy |
| Rating(kw) | | |
| Voltage(volts) | | |
| Current(amps) | | |

PROCEDURE:

1. Connect the circuit as shown in the diagram.
2. Switch on the single phase a.c. supply.
3. Record the voltages V_1 , V_2 and V_3 . In case $V_3 < V_1$ polarity is subtractive.
4. Repeat the step 3 after connecting terminals as shown in figure of additive polarity. In case $V_3 > V_1$ polarity is additive.
5. Switch off the a.c. supply.

TABULATION:**SUB-POLARITY**

| S.No | V_1 (volts) | V_2 (volts) | $V_3 = V_2 - V_1$ (volts) |
|------|---------------|---------------|---------------------------|
| | | | |

ADD-POLARITY

| S.No | V_1 (volts) | V_2 (volts) | $V_3 = V_1 + V_2$ (volts) |
|------|---------------|---------------|---------------------------|
| | | | |

RESULT:

Thus the polarity of a single phase transformer was determined.

VIVA QUESTIONS:

1. Why correct polarity is important in parallel operation of transformers?
2. What are the different types of testing of transformer?
3. What is polarity test in transformer?
4. Compare two winding transformer and auto transformer.
5. Is possible for any voltage winding in a transformer to serve as its primary?

| | | |
|----------|--|---|
| Ex. No : | | SUMPNER'S TEST ON SINGLE PHASE TRANSFORMER |
| Date : | | |

AIM:

To predetermine the percentage efficiency and percentage regulation of the given two identical single phase transformers by conducting Sumpner's test or back to back test.

FUSE RATING:

Primary rated current = $\frac{\text{kVA rating}}{\text{Primary voltage}}$

Secondary rated current = $\frac{\text{kVA rating}}{\text{Secondary voltage}}$

OPEN CIRCUIT TEST:

25% of rated L.V. winding current= _____ amps.

SHORT CIRCUIT TEST:

125% of rated HV winding current= _____ amps.

APPARATUS REQUIRED:

| S.No | Name of the equipment | Type | Range | Quantity |
|------|-----------------------|-------------------------|---------------------|----------|
| 1 | Ammeter | Moving Iron(MI) | (0-2)amps | 1 |
| 2 | Ammeter | Moving Iron(MI) | (0-10)amps | 1 |
| 4 | Voltmeter | Moving Iron(MI) | (0-150)volts | 1 |
| 5 | Voltmeter | Moving Iron(MI) | (0-300)volts | 2 |
| 6 | Voltmeter | Moving Iron(MI) | (0-75)volts | 1 |
| 7 | Wattmeter | Low power factor(LPF) | (300volts,2.5amps) | 1 |
| 8 | Wattmeter | Unity power factor(UPF) | (150volts,10amps) | 1 |
| 9 | Auto transformer | 1Phase | 230/(0-270) volts | 2 |
| 10 | Transformer | 1Phase | 2kVA,(230/230)volts | 2 |
| 11 | Connecting wires | - | - | Required |

FORMULAE:

W_1 connected in the circuit of the primaries measures the total core losses of both the transformers

Then the iron losses of each transformer = $\frac{1}{2} W_0$ ($\because W_1 = W_0$)
= W_1

W_2 is connected in the secondary circuit measures the total full load copper losses of the two transformers.

Hence, full load copper losses of each transformer $W_{cu} = \frac{1}{2} W_{sc}$ ($W_2 = W_{sc}$)

EFFICIENCY AT FULL LOAD:

Let the output is KVA of each transformer be P_0

Total losses of each transformer under full load operation = $\frac{1}{2} W_0 + \frac{1}{2} W_{cu}$

Percentage efficiency at full load = $\frac{P_0 * 1000 * \cos\phi * 100}{P_0 * 1000 * \cos\phi + \frac{1}{2} W_0 + \frac{1}{2} W_{cu}}$

$P_0 * 1000 * \cos\phi + \frac{1}{2} W_0 + \frac{1}{2} W_{cu}$

| S. No | Load (amps) | Copper loss (watts) | Constant loss (watts) | Total loss (watts) | O/p (watts) | % η |
|-------|-------------|---------------------|-----------------------|--------------------|-------------|----------|
| | | | | | | |
| | | | | | | |

PRECAUTION:


- The autotransformer must be kept at minimum potential position at the time of starting.

DESCRIPTION:

Sumpner's or back to back test provides the data for finding the regulation, efficiency and heating under load conditions and is employed only when two identical transformers are available. One transformer is loaded on the other and both are connected to supply. The power taken from the supply is that necessary for supplying the losses of both transformers and the negligibly small loss in the control circuit.

PROCEDURE:

1. The nameplate details are noted down and the range of meters selected is justified.
2. Connections are made as per the circuit diagram
3. Observing the precautions, the DPST switch is closed.
4. Autotransformer is adjusted to set rated primary voltage
5. Now, the voltage across the secondaries must read zero. in case the voltage reads twice the rated voltage of each transformer, the DPST switch is opened and the connection at the secondary terminals of one of the transformers is interchanged.
6. Now, close the other two switches.
7. The autotransformer is adjusted so that the current flowing in the secondaries is full load secondary current of each transformer.
8. All the meter readings are noted down.
9. The DPST switches are opened.

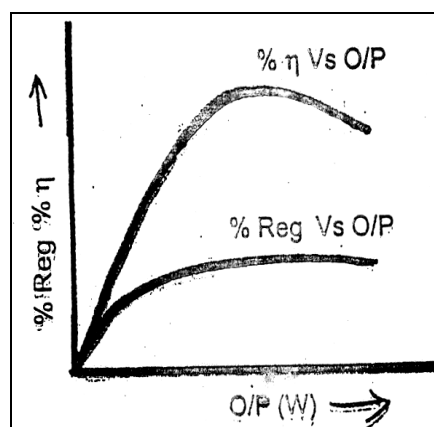MODEL GRAPH:

CALCULATIONS:**RESULT:**

Thus the Sumpner's test was conducted on two identical transformers and the efficiency was found out at different loaded conditions.

VIVA QUESTIONS:

1. What are the advantages of back to back test in determining efficiency of a transformer?
2. Why the iron losses are constant at all loads in a transformer?
3. What would happen if a power transformer designed for operation on 50 Hz were connected to 5Hz of the same voltage?
4. What is a current transformer?
5. What is a potential transformer?

| | | |
|-----------------|--|---|
| Ex. No : | | SEPARATION OF NO LOAD LOSSES IN SINGLE PHASE TRANSFORMER |
| Date : | | |

AIM:

To separate the no load losses in the given transformer as Hysteresis and eddycurrent losses at a given frequency.

APPARATUS REQUIRED:

| S.No | Name of the equipment | Type | Range | Quantity |
|------|-----------------------|------------------------|--------------------|----------|
| 1 | Voltmeter | Moving Iron(MI) | (0-300) volts | 1 |
| 2 | Rheostat | Wire Wound | (300ohms,2amps) | 1 |
| 4 | Rheostat | Wire Wound | (230ohms,1.7amps) | 1 |
| 5 | Rheostat | Wire Wound | (100 ohms,4amps) | 1 |
| 6 | Wattmeter | Low power factor (LPF) | (300volts,2.5amps) | 1 |
| 7 | Transformer | inductive | 230/230 volts | 1 |

FORMULAE:

Frequency, $f = (P * N_s) / 120$ in Hertz

P = No.of Poles & N_s = Synchronous speed in rpm.

Hysteresis Loss $W_h = A * f$ in Watts A = Constant (obtained from graph)

Eddy Current Loss $W_e = B * f^2$ in Watts B = Constant (slope of the tangent drawn to the curve)


Iron Loss $W_i = W_h + W_e$ in Watts

$$W_i / f = A + (B * f)$$

Here the Constant A is distance from the origin to the point where the line cuts the Y- axis in the graph between W_i / f and frequency f.

The Constant B is $\Delta(W_i / f) / \Delta f$

CIRCUIT DIAGRAM:

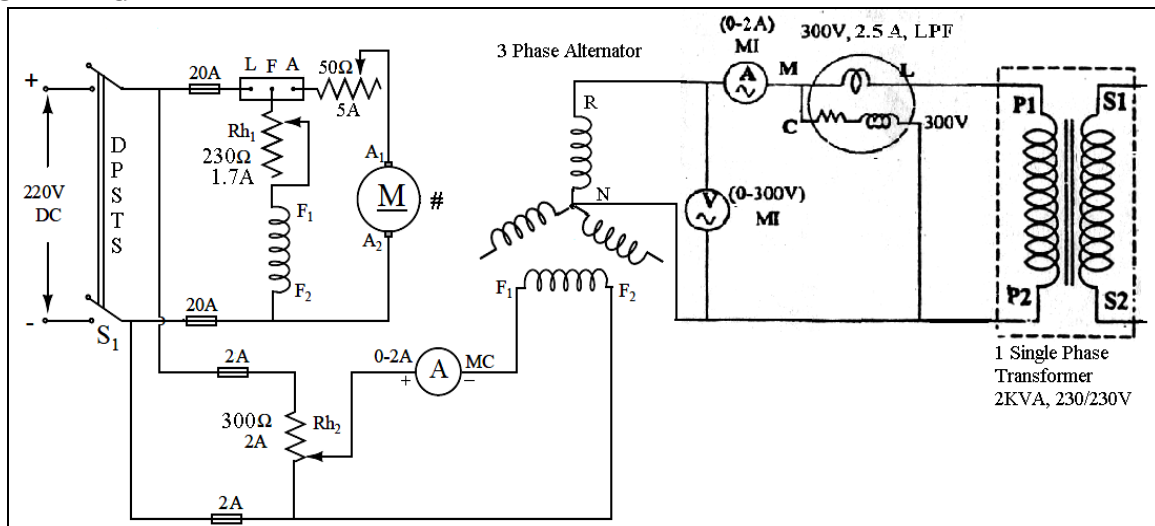

NAME PLATE DETAILS

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

| PARAMETER | TRANSFORMER | | DC MOTOR | ALTERNATOR |
|----------------|-------------|------|----------|------------|
| | Py | Sy | | |
| Rating(kw) | | | | |
| Voltage(volts) | | | | |
| Current(amps) | | | | |
| Speed(rpm) | ---- | ---- | | |
| Excitation | ---- | ---- | | |

PRECAUTIONS:

- The potentiometer connected to a alternator field is at minimum voltage position(zerovoltage)
- The field rheostat of DC motor field is kept at minimum position.
- The rheostat connected to DC motor armature is kept at minimum resistance position.
- The HV side of transformer is connected between any one of the terminals of alternator and neutral.

DESCRIPTION:

Consider a practical transformer on no load i.e. the secondary of the transformer is kept open. The primary will draw a small current I_0 to supply (i)iron losses (ii)a very small amount of copper loss in the primary.No load input power, $W_0=V_1I_0 \cos\phi$.

At no load, copper loss in the primary is I_0^2R .since I_0 is very small, this loss is neglected. Therefore the no load primary input power is practically equal to the iron loss in the transformer.



PROCEDURE:

1. Connections are made as per the circuit diagram shown in fig.
2. Observing the precautions the DPST switch is closed.
3. The internal resistance connected to armature is decreased gradually and brought to minimum resistance position.
4. The field rheostat is adjusted to get rated speed of the motor
5. The field rheostat of alternator is adjusted to get rated voltage of transformer.
6. The readings are observed at rated speed of motor and rated voltage of transformer, initially and the ratio (V/N) is maintained constant as shown in table.
7. Now the rheostat connected to armature is adjusted to vary the frequency of alternator.
8. The readings are observed at constant (V/N) .the field rheostat of alternator is adjusted to maintain (V/N) constant.
9. The equipments are brought back to their original position and supply is switched off.

TABULATION:

| S.No | Speed N | Voltage V | Power W_1 | | Frequency f | W_i/f |
|------|------------|--------------|-------------|--------|----------------|---------|
| | | | Observed | Actual | | |
| | rpm | volts | watts | watts | Hertz(Hz) | W/Hz |
| | | | | | | |
| | | | | | | |
| | | | | | | |
| | | | | | | |
| | | | | | | |

| S.No | $A \cdot 10^{-2}$ meter | $W_h = A_f$ (watts) | $B \cdot 10^{-2}$ meter | $W_e = B_f^2$ (waats) | F (Hz) |
|------|-------------------------|---------------------|-------------------------|-----------------------|--------|
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |

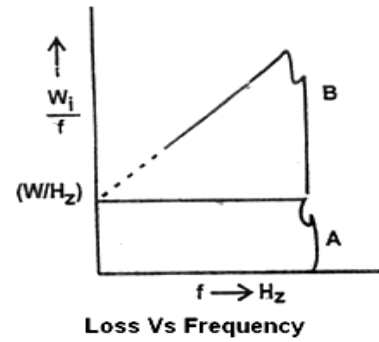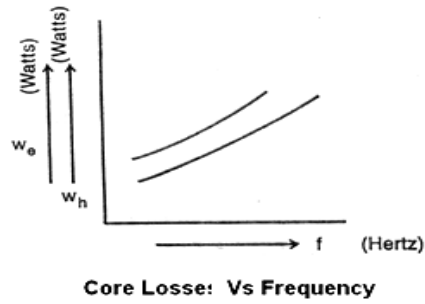MODEL GRAPH:**CALCULATIONS:****RESULT:**

Thus the core losses were separated and the corresponding curves were drawn.

VIVA QUESTIONS:

1. What are the losses in a transformer?

2. What is meant by core losses?

3. What is meant by Hysteresis losses?

4. What is meant by eddy current losses?

5. What are the methods to reduce the losses?

Ex. No :

Date :

STUDY OF THREE PHASE TRANSFORMER CONNECTIONS**AIM:**

To study the three phase transformer connections in
 (i) star-star (ii) delta-star (iii) delta-delta (iv) star-delta.

DESCRIPTION:


The necessity of the three phase system in generation, transmission and distribution is well known to us. Combination of the electrical system and the electromagnetic system of three identical single phase transformers into a single system makes it possible to get a three phase transformer as a single unit, therefore it is interesting to study the different connections in different possible manners.

THEORY OF 3-PHASE TRANSFORMER CONNECTIONS:

- (i) Primary in star and secondary in star
- (ii) Primary in delta and secondary in star
- (iii) Primary in delta and secondary in delta
- (iv) Primary in star and secondary in delta.

PROCEDURE:

1. Connect the circuit connections as shown in the fig.
2. Measure the line voltage and phase voltages and tabulate as shown in the table.
3. For a ratio of 'n' and primary line voltage 'v' the various phase and line voltages will be as shown in the table, actual values would be furnished in table.

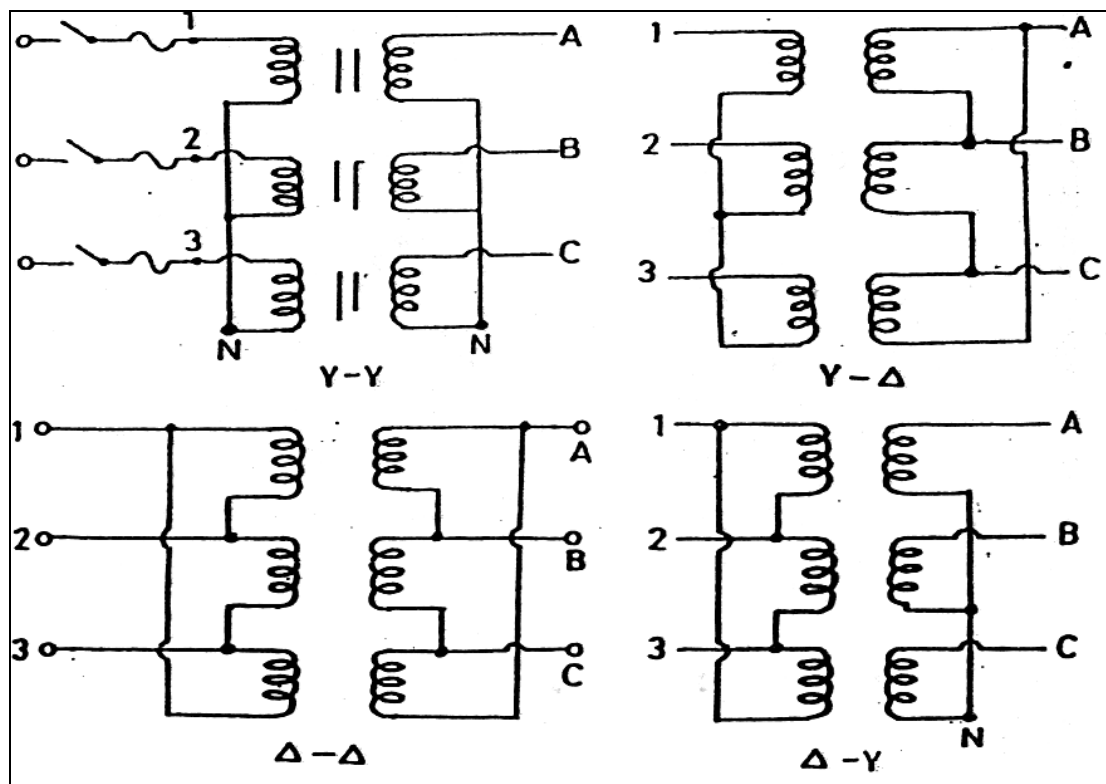CONNECTION DIAGRAM:

Connection diagrams of three transformers

TABULATION:

| Tabulation For Transformer Connection-various line and phase voltages | | | | | | | | | | | | | |
|---|-----------|------------------------|-----------------|-----------------|-------------------------|-----------------|------------------------|------------------------|---------------------|---------------------|-------------------------|-----------------|-----------------|
| | | Primary voltages (V) | | | | | Secondary voltages (V) | | | | | | |
| Primary | Secondary | Line Voltages in volts | | | Phase Voltages in volts | | | Line Voltages in volts | | | Phase Voltages in volts | | |
| | | V ₂₃ | V ₁₂ | V ₃₁ | V _{1N} | V _{2N} | V _{3N} | V _{AB} | V _{BC} | V _{CA} | V _{AN} | V _{BN} | V _{CN} |
| Star | Star | V | V | V | $V/\sqrt{3}$ | $V/\sqrt{3}$ | $V/\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V/\sqrt{3}$ | $V/\sqrt{3}$ | $V/\sqrt{3}$ |
| Star | Delta | V | V | V | $V/\sqrt{3}$ | $V/\sqrt{3}$ | $V/\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V/\sqrt{3}$ | $V/\sqrt{3}$ | $V/\sqrt{3}$ |
| Delta | Delta | V | V | V | V | V | V | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ |
| Delta | Star | V | V | V | V | V | $\sqrt{3}V\sqrt{3}$ | $\sqrt{3}V\sqrt{3}$ | $\sqrt{3}V\sqrt{3}$ | $\sqrt{3}V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ | $V\sqrt{3}$ |

| Tabulation For Transformer Connection-various line and phase voltages | | | | | | | | | | | | | |
|---|-----------|------------------------|-----------------|-----------------|-------------------------|-----------------|------------------------|------------------------|-----------------|-----------------|-------------------------|-----------------|-----------------|
| | | Primary voltages (V) | | | | | Secondary voltages (V) | | | | | | |
| Primary | Secondary | Line Voltages in volts | | | Phase Voltages in volts | | | Line Voltages in volts | | | Phase Voltages in volts | | |
| | | V ₂₃ | V ₁₂ | V ₃₁ | V _{1N} | V _{2N} | V _{3N} | V _{AB} | V _{BC} | V _{CA} | V _{AN} | V _{BN} | V _{CN} |
| Star | Star | | | | | | | | | | | | |
| Star | Delta | | | | | | | | | | | | |
| Delta | Delta | | | | | | | | | | | | |
| Delta | Star | | | | | | | | | | | | |

RESULT:

Thus the phase transformer connections were studied.

VIVA QUESTIONS:

1. The three phase system has only two types of connections viz. star connection and delta connection. Why?
2. What are the advantages and disadvantages of three phase transformer over three single phase transformer?
3. List the applications of transformers.
4. Can 50 Hz Transformers be used at Higher Frequencies?
5. What will happen if the primary of a transformer is connected to dc supply?

Ex. No :

Date :

LOAD CHARACTERISTICS OF DC SERIES GENERATOR


AIM:

To draw the load characteristics of DC series generator by conducting load test on it.

APPARATUS REQUIRED:

| S.NO. | APPARATUS REQUIRED | TYPE | RANGE | QUANTITY |
|-------|--------------------|-----------------|------------------------|----------|
| 1 | Ammeter | Moving coil(MC) | (0-20)amps | 1 |
| 2 | Voltmeter | Moving coil(MC) | (0-300)volts | 1 |
| 3 | Rheostat | Wire wound | 230 Ω , 1.7amps | 1 |
| 4 | Resistive load | - | 3kw | 1 |
| 5 | Tachometer | Digital | - | 1 |
| 6 | Connecting wires | - | - | Req |

CIRCUIT DIAGRAM:

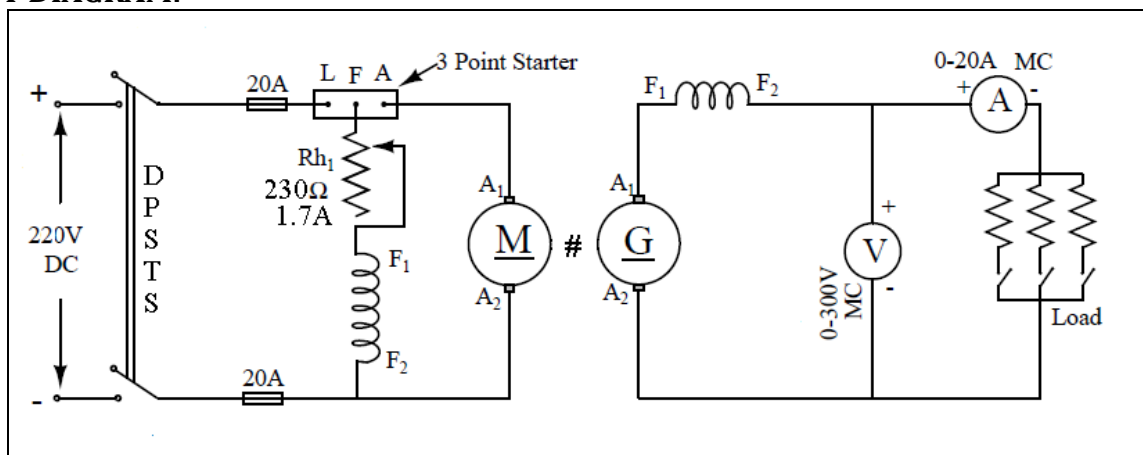

FUSE RATING:

For Load Test Fuse Rating=125% of rated current.

NAME PLATE DETAILS

| PARAMETER | DC SHUNT MOTOR |
|----------------|----------------|
| Rating(kw) | |
| Voltage(volts) | |
| Current(amps) | |
| Speed(rpm) | |

FORMULAE:

$$E_g = V + I_a R_a \text{ (Volts)}$$

$$I_L = I_a + I_f \text{ (amps)}$$

$$R_a = \frac{V_a}{I_a} \text{ ohms}$$

Where

E_g - Generated emf at load condition in volts V - Terminal voltage in volts

I_a - Armature resistance in ohm

I_L - Load current in amps

I_f - Field current in amps

V_a - Armature voltage in volts

PRECAUTIONS:


- All the Double Pole Single Through (DPST) switch should be kept open
- Motor field rheostat should be in minimum position only
- All the switches in resistive load should be in off position
- In the measurement of armature resistance, rheostat should be in maximum resistance position.

PROCEDURE:**LOAD TEST:**

1. Make the connection as per the circuit diagram
2. Close the DPST switch1
3. Start the motor using three point starter.
4. By adjusting motor field rheostat set the motor-generator to its rated speed
5. Now close the DPST switch2.
6. Adjust the resistive load and note down the corresponding load current I_L and terminal voltage indicated by the ammeter and voltmeter respectively.
7. Repeat the same procedure till the load current reaches the rated load current

TABULATION

| S.No. | Load current (I_L in amps) | Terminal voltage (V_t in volts) | Generated voltage (E_g in volts) |
|-------|-------------------------------|------------------------------------|-------------------------------------|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

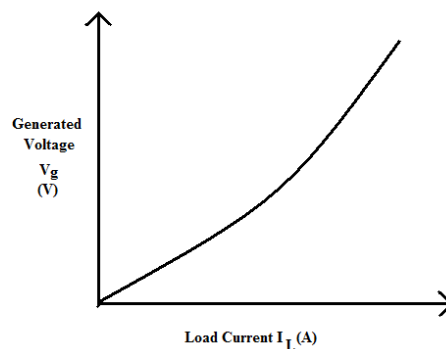MODEL GRAPH:

Graph Representing the Load Characteristics of DC Series Generator.

CALCULATIONS:**RESULT:**

Thus the load test was conducted on DC series generator and the performance curve was drawn.

VIVA QUESTIONS:

1. Why series generator not generally used?
2. What does the name plate of a DC generator generally indicate?
3. Which losses occur in a DC generator?
4. Why the field winding of a series DC machine does has less number of turns than that of DC shunt machine?
5. Why is the efficiency of a DC generator not determined by direct loading?

Observation

Roll No.:

| S. No. | Date | Title | Page No. | Teacher's Sign/Remarks |
|--------|---------|---|----------|------------------------|
| 1. | 22/8/22 | LOAD TEST ON DC SHUNT MOTOR | 2 | (10) P. Ummy 3/9/22 |
| 2. | 24/8/22 | LOAD TEST ON DC SERIES MOTOR. | 7 | (10) P. Ummy 3/9/22 |
| 3. | 3/9/22 | SPEED CONTROL OF DC SHUNT MOTOR. | 10 | (10) P. Ummy 3/9/22 |
| 4 | 14/9/22 | LOAD TEST ON SINGLE PHASE TRANSFORMER | 14 | (10) P. Ummy |
| 5 | 24/8/22 | LOAD TEST ON DC COMPOUND MOTOR | 19 | (10) P. Ummy |
| 6 | 14/9/22 | Open Circuit & Load Characteristics of DC shunt generator = Critical resistance | 22 | (10) P. Ummy |

| S.No | Date | Title | Page. | Mark | Signature |
|------|----------|---|-------|------|-----------|
| 7 | 14/9/22 | Stuenkel's Test | 24 | (10) | P. Ummy |
| 8 | 28/11/22 | Load characteristics of DC compound generator with different and cumulative connections | 26 | (10) | P. Ummy |
| 9 | 7/12/22 | open circuit test and short circuit test on single phase transformer | 28 | (10) | P. Ummy |
| 10 | 1/12/22 | harkinsons test on DC motor-generator | 30 | (10) | P. Ummy |
| 11 | 7/9/22 | Load test on three phase transformer | 32 | (10) | P. Ummy |
| 12 | 15/12/22 | Determination of on load losses in single phase transformer | 34 | (10) | P. Ummy |

Completed
P. Ummy



A NAAC Accredited Institution
KINGS
COLLEGE OF ENGINEERING
Recognized under 2(f) & 12(B) of UGC
Approved by AICTE, New Delhi
Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

BONAFIDE CERTIFICATE

Register Number: 821121105014

This is to certify that, the record work was done by the candidate Mr./Ms. K. BUTHBAN of II Year, III Semester, B.E. Electrical and Electronics Engineering for **EE3311 - Electrical Machines Laboratory- I** during the academic year 2022-2023 (Odd Semester).

P. Narasimhan
20/11/23
Staff in-Charge

P. Narasimhan
20/11/23
Head of the Department

This record is submitted for Anna University, Chennai, practical examination held on 30/01/2023 at Kings College of Engineering, Punalkulam.


P. Narasimhan
30/11/23
Internal Examiner

P. Narasimhan
30/01/23
External Examiner

INDEX

EE3311 - Electrical Machines Laboratory- I

| Ex. No | Date | Title of the Experiment | Page No. | Mark | Signature |
|---------------------------|------------|--|----------|------|---------------|
| 1(a) | 22/08/22 | Study of DC Motor starter | 76 | (10) | P. N. Jeyaraj |
| 1(b) | 22/08/22 | Study of three phase transformer connections | 82 | (10) | P. N. Jeyaraj |
| 2. | 22/08/22 | Speed control of DC shunt motor | 13 | (10) | P. N. Jeyaraj |
| 3. | 24/08/22 ✓ | Load test on DC shunt motor | 2 | (10) | P. N. Jeyaraj |
| 4. | 08/09/22 ✓ | Load test on DC series motor | 8 | (10) | P. N. Jeyaraj |
| 5. | 04/09/22 | Load test on single phase transformer | 20 | (10) | P. N. Jeyaraj |
| 6. | 07/09/22 | Load test on three phase transformer | 64 | (10) | P. N. Jeyaraj |
| 7. | 14/09/22 ✓ | Swinburn's test | 38 | (10) | P. N. Jeyaraj |
| 8. | 21/09/22 ✓ | Open circuit and load characteristic of DC shunt generator - critical resistance & speed | 32 | (10) | P. N. Jeyaraj |
| 9. | 28/11/22 ✓ | Load characteristic of DC compound generator with differential & cumulative connection | 44 | (10) | P. N. Jeyaraj |
| 10. | 28/11/22 ✓ | Load test on DC compound motor | 26 | (10) | P. N. Jeyaraj |
| 11. | 1/12/22 | Hopkinson's test on DC motor, generator set | 58 | (10) | P. N. Jeyaraj |
| 12. | 7/12/22 | Open circuit & short circuit test on single phase transformer | 50 | (10) | P. N. Jeyaraj |
| 13. | 15/12/22 | Swamp's test on single phase transformer | 86 | (10) | P. N. Jeyaraj |
| 14. | 17/12/22 | Separation of no load losses in single phase transformer | 70 | (10) | P. N. Jeyaraj |
| [Content Beyond Syllabus] | | | | | |
| 15 | 19/12/22 | Load characteristics of DC series generator | 92 | — | P. N. Jeyaraj |

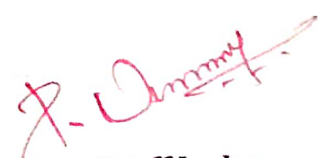
 Signature of Staff Incharge

B.E / B.Tech. PRACTICAL END SEMESTER EXAMINATIONS, NOVEMBER/DECEMBER 2022

Third Semester

EE3311 - ELECTRICAL MACHINES LABORATORY - I

Regulation s 2021

Time : 3 Hours

Max. Marks 100

| Aim/Principle/Apparatus required/Procedure | Tabulation/Circuit/ Program/Drawing | Calculation & Results | Viva-Voce | Record | Total |
|---|--|----------------------------------|------------------|---------------|--------------|
| 20 | 30 | 30 | 10 | 10 | 100 |

1. Conduct the following experiment on the given DC machine whose field and armature windings are connected in parallel
 - i obtain the magnetization characteristics at 1250 rpm
 - ii critical speed of the given machine.
2. Conduct a suitable experiments on the given DC generator in which the field and armature windings are connected in parallel and is excited by a DC source. Plot the terminal characteristics of the machine.
3. Obtain the load characteristics of the DC machine which delivers electrical power when the flux produced by both the field winding aid each other.
4. Obtain the load characteristics of the DC machine which delivers electrical power when the flux produced by both the field winding oppose each other.
5. Obtain the following performance characteristics at 25%, 50%, 75% and 100 % of the given DC machine which converts electrical energy into mechanical energy and having constant speed
 - i Output power Vs speed
 - ii Output power Vs efficiency

6. Obtain the mechanical characteristics of the given DC machine which converts electrical energy into mechanical energy. The DC machine has both shunt field and series field winding.
7. Obtain the mechanical characteristics of the given DC machine which converts electrical energy into mechanical energy and the machine has the higher starting torque.
8. Conduct a suitable test on the given DC machine and pre determine its efficiency while operating as motor and generator.
9. Obtain the flux control characteristics of the given DC shunt motor when its armature voltage is i $V_a = V_r$ and ii $V_a = 0.8 V_r$ also explain the function of three point starter.
10. Obtain the rheostatic control characteristics of the given DC shunt motor when its field current is i $I_f = I_{fn}$ and ii $I_f = 1.1 I_{fn}$ also explain the function of four point starter.
11. Conduct a suitable test on the given two identical machines and determine their efficiency as motor and generator.
12. Conduct a suitable test on the given single phase static device and determine the performance characteristic curve.
13. Conduct a suitable test on the given three phase static device and determine the performance characteristic curve.
14. Obtain the equivalent circuit parameters for the given single phase static device which works on the principle of mutual induction referred to supply side.
15. By conducting a suitable test on the given pair of identical transformers plot the performance characteristic curve.
16. By conducting a suitable test on the given static device, separate the iron loss components when it is operating at rated voltage on 50 Hz. Supply.
17. By conducting a suitable test on the given single phase static device draw the load characteristics at 50%, 75%, 100% and 125 % of loading and determine the efficiency of the device.

18. By conducting a suitable test on the given static device find the eddy current loss and hysteresis loss when it is operating at rated voltage on 50 Hz. Supply.
19. Conduct a load test on the given static three phase machine which works under the principle of mutual induction and plot the characteristics curve also draw the various combinations of its connection.
20. By conducting a suitable test on the given DC machine obtain the speed control characteristics by i field control method and ii armature resistance control method.



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Model Lab Exam - Mark Statement

Year /Sem: II/III

Staff Name: Dr.P.Narasimman

Subject Name: Electrical Machines -I Lab

Subject Code: EE3311

Date:19.12.2022

| S. NO. | STUDENT NAME | MARKS |
|--------|---------------------|-------|
| 1 | ABIBHARATHI A | 81 |
| 2 | AKASH P | 77 |
| 3 | ARAVINDHAN R | 78 |
| 4 | DHESINGH J | 76 |
| 5 | GAYATHRI K C | 92 |
| 6 | GOKUL M | 85 |
| 7 | GOPINATH S | 87 |
| 8 | HARISHMA R | 84 |
| 9 | JEGADEESAN R | 86 |
| 10 | KARTHIKEYAN S | 82 |
| 11 | MEENA P | 84 |
| 12 | MILTON INFANT RAI P | 88 |
| 13 | PRAVEEN V C | 75 |
| 14 | RUTHRAN K | 93 |
| 15 | SARAVANAKUMAR M | 82 |
| 16 | SHANMUGAESWARAN S | 83 |
| 17 | SIVANANTHAM S | 85 |
| 18 | SIVANESAN C | 88 |
| 19 | SUJITHA S | 85 |
| 20 | SURIYA G | 82 |
| 21 | THAVATHEESH S | 83 |
| 22 | THUSARI S | 89 |
| 23 | VAISHNAVI V | 84 |
| 24 | VIDHYA M | 88 |
| 25 | VIJAY V | 84 |

| S. NO. | STUDENT NAME | MARKS |
|--------|-------------------|-------|
| 26 | YOGESH C | 79 |
| 27 | YUVARAJ A | AB |
| 28 | MONISHAN A | 76 |
| 29 | PARTHASARATHY B | 81 |
| 30 | PANDIYARAJAN R | 80 |
| 31 | PRAGADEESHWARAN S | 79 |
| 32 | VEERASELVAN V | 87 |
| 33 | UDHAYAM S | 83 |

P. Narasimman
19/12/22.
Staff Incharge

A. Arumugam
19/12/22
HoD/EEE

MODEL LAB Exam

NAME: M. Gokul

Roll NO: 21EE06

Reg NO: 821121105006

Date: 19/12/2022

Subject code: EE3311

Date: 19.12.2022



Subject NAME: Electrical Machines I

| S. N | Description | Mark | obtained marks |
|------|-------------------------------|------|--------------------------------|
| 1. | AFM, Apparatus Required | 10 | 10 |
| 2. | Circuit diagram | 30 | 25 |
| 3. | Procedure, connection diagram | 30 | 27 |
| 4. | Result, graph | 20 | 17 |
| 5. | VIVA - VPCE | 10 | 06 85 |

Internal Examiner

External Examiner

(Signature)

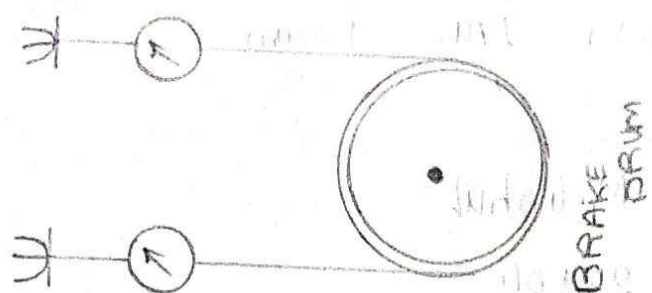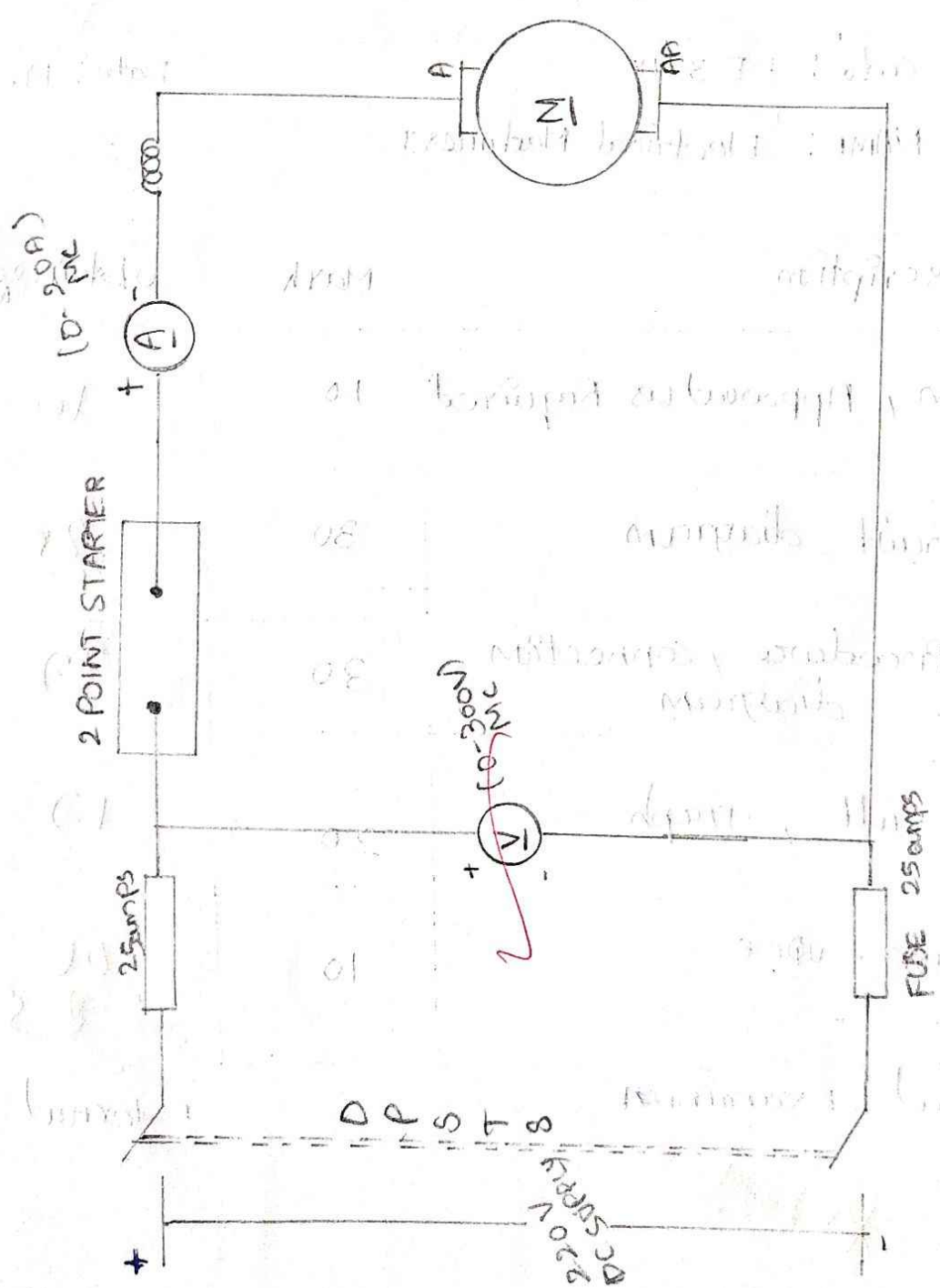

| PARAMETER | DESERIES MOTOR |
|-----------------|----------------|
| Rating (Kw) | 3.5 Kw |
| Voltage (Volts) | 220 Volts |
| Current (amps) | 20.00amps |
| Speed (rpm) | 1500rpm |

Name Plate Details
Fuse Rating

For load test Fuse Rating = 125% of rated current

Aim:

To conduct the load test on a given DC series motor and to draw its performance curves

Apparatus Required

| S. No | Name of the Apparatus | Type | Range | Quantity |
|-------|-----------------------|------------------|---------------|----------|
| 1. | Ammeter | Moving coil (MC) | (0-20) amp | 1 |
| 2. | volt meter | Moving coil (MC) | (0-300) volts | 1 |
| 3. | Tachometer | Digital | - | 1 |
| 4. | Connecting wires | - | - | Req |

Formula:-

For load test fuse Rating = 125% of rated current

$$\text{Torque } T = (S_1 - S_2) \times \left(R + \frac{t}{2}\right) \times 9.81 \text{ N/m}$$

where R - radius of brake drum in m

t - thickness balance reading in kg

$$\text{Input power } P_i = V_L I_L \text{ watts}$$

TABULATION

OBSERVATION: Radius of a brake drum = m

| S. No | V _a (volts) | I _L (amps) | I _F (amps) | N (rpm) | Spring Balance | | S ₁ -S ₂ (kg) | Torque (N-m) | Input (watts) | output (watts) | Efficiency |
|-------|------------------------|-----------------------|-----------------------|---------|----------------|----------------|-------------------------------------|--------------|---------------|----------------|------------|
| | | | | | S ₁ | S ₂ | | | | | |
| 1. | 210 | 6.8 | | 2841 | 8 | 4 | 4 | 4.28 | 1428.0 | 1272.69 | 89.18 |
| 2. | 208 | 9.0 | | 2209 | 16 | 10 | 6 | 6.42 | 1872.0 | 1484.35 | 79.29 |
| 3. | 204 | 11.4 | | 1936 | 20 | 15 | 5 | 5.35 | 2325.6 | 1004.09 | 46.61 |
| 4. | 22 | 14.8 | | 1842 | 25 | 20 | 5 | 5.35 | 29866 | 1031.45 | 34.50 |
| 5. | 200 | 18.0 | | 1475 | 32 | 24 | 8 | 8.56 | 3600.0 | 1321.52 | 36.70 |

where, V_L = load voltage in V

I_L = load current in A

$$\text{output power, } P_o = \frac{2\pi NT}{60} \text{ Watts}$$

where N - speed of the armature in rpm

T - Torque in Nm

$$\% \text{ Efficiency} = \frac{\text{Output Power}}{\text{Input Power}} \times 100$$

PRECAUTIONS:

* The motor field rheostat should be kept at minimum resistance position.

* At the time of starting the motor should be in no load condition.

* The motor should be run in anticlockwise direction.

PROCEDURE:

* Connections are given as per the circuit diagram.



* Initially apply some load.

* Using the two point starter the motor is started to run.

* The meter readings are noted.

* By using the break with spring balance arrangement the motor is loaded and the corresponding readings are noted up to the rated current.

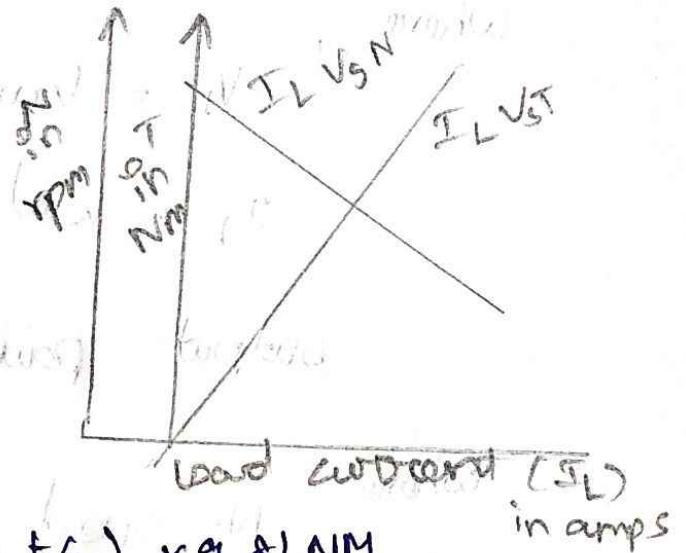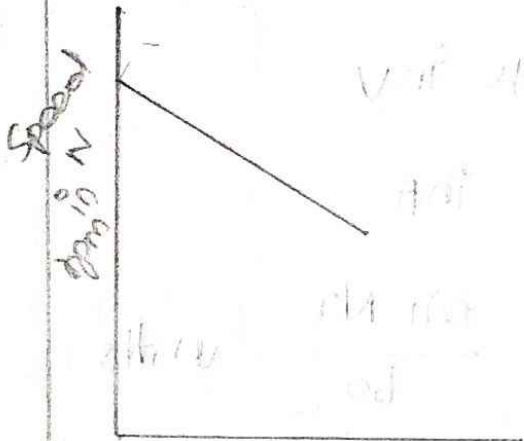* After the observation of all the readings the load is released gradually not fully.



output Torque (T), in N-m

$$\begin{aligned} \text{Torque} &= (S_1 - S_2) \times (R + t/2) \times 9.81 \text{ NM} \\ &= (32 - 24) \times (0.1066 + 0.0025) \times 9.81 \\ &= 8 \times 0.1091 \times 9.81 \\ \text{Torque (T)} &= 8.56 \text{ NM} \end{aligned}$$

$$\text{output power } P_o = \frac{2\pi NT}{60} \text{ watts}$$

$$= \frac{2 \times 3.14 \times 1475 \times 8.56}{60}$$

$$= \frac{79.291 \cdot 28}{60}$$

$$= 1321.52 \text{ watts}$$

$$\text{Input power } P_i = V_L I_L$$

$$= 200 \times 18$$

$$= 3600 \text{ watts}$$

$$\% \text{ Efficiency} = \frac{\text{output Power}}{\text{Input Power}} \times 100$$

$$= \frac{1321.52}{3600} \times 100$$


$$= 0.3670 \times 100$$

$$= 36.70\%$$


Mechanical characteristics

Scale

1 cm = 1000 rpm
1 cm = 500 N·m

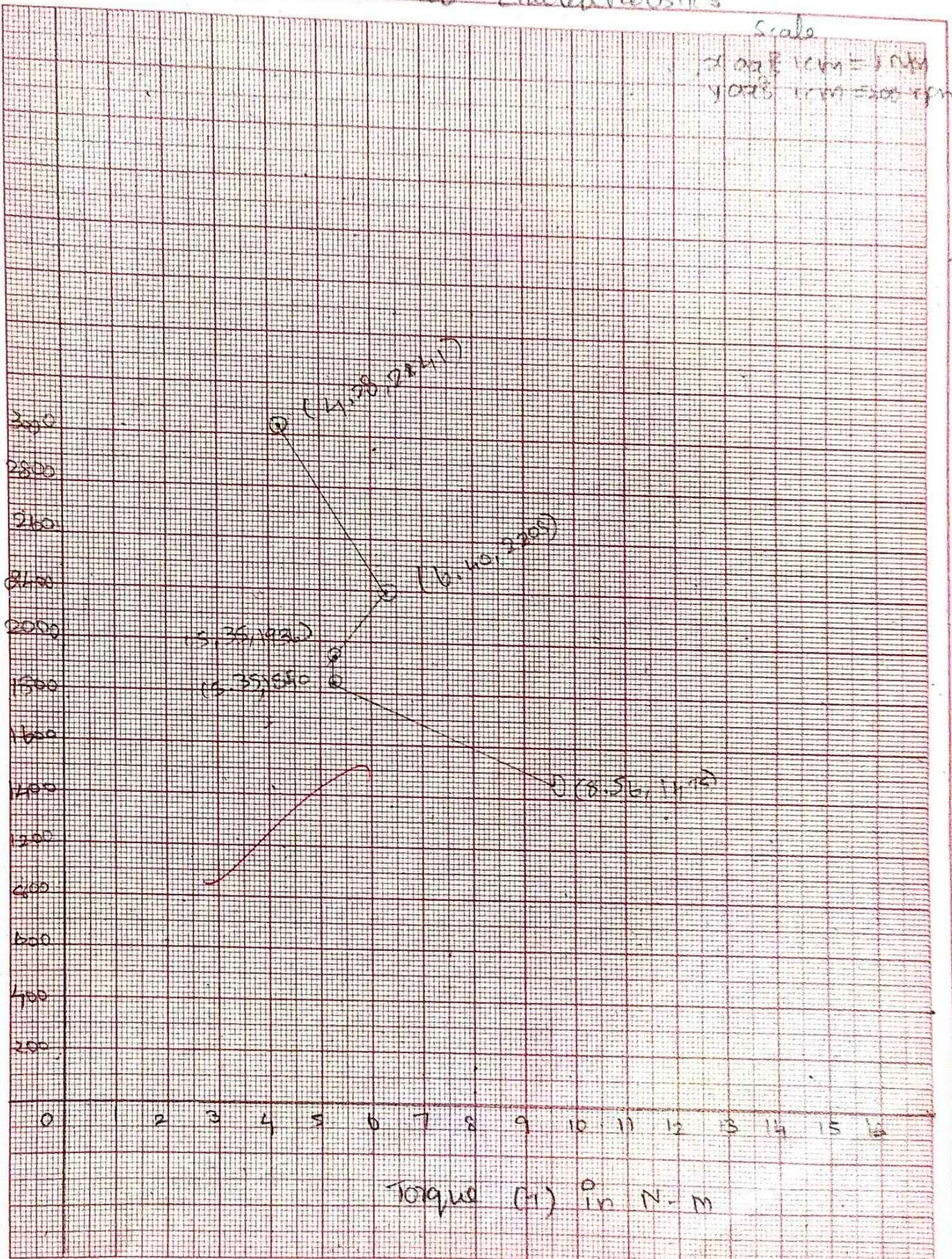

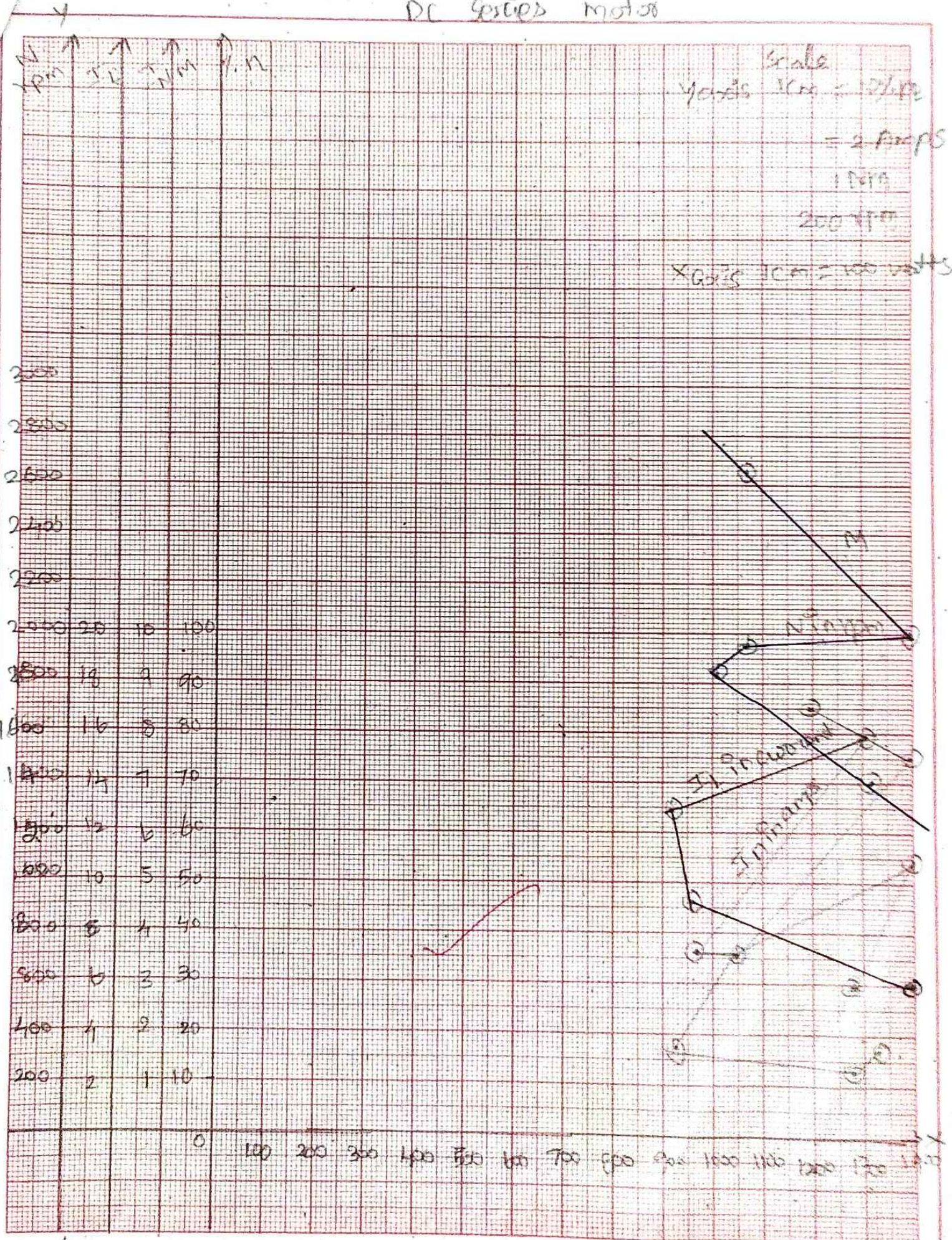
The load characteristics of DC series motor




electrical characteristics

Scale

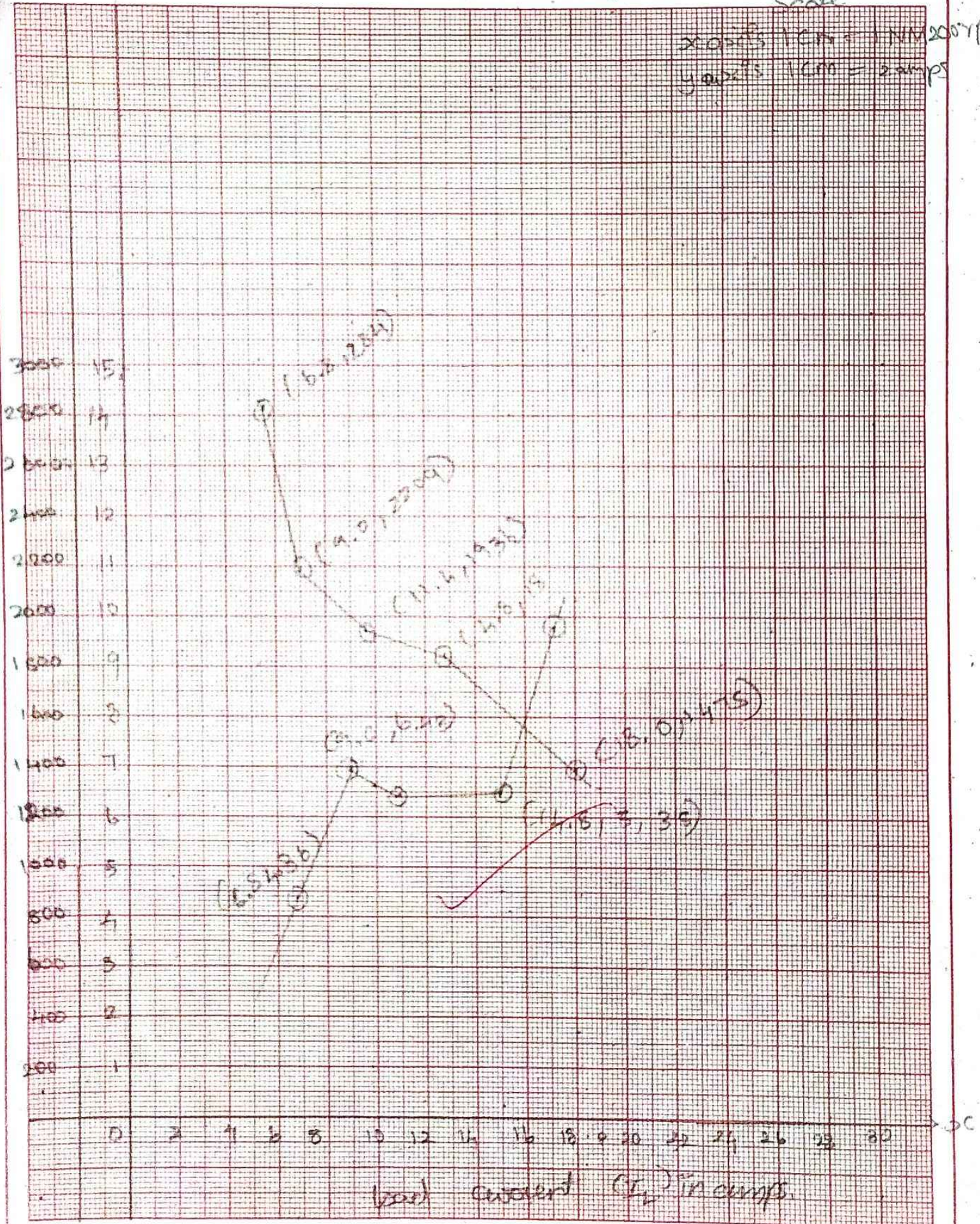x-axis: 1cm = 1NM 20078
y-axis: 1cm = 2amps




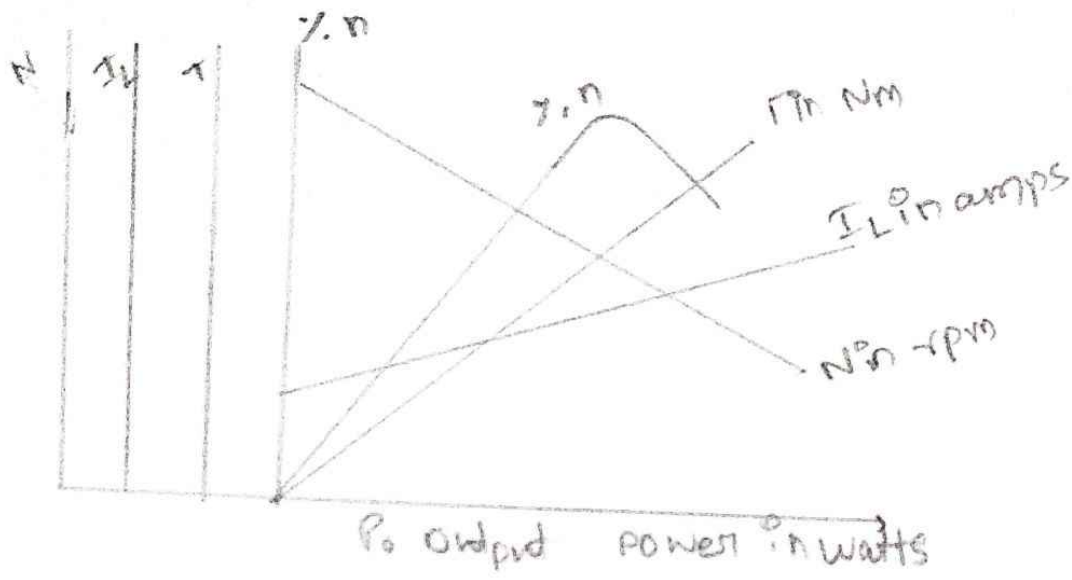

P. Jimmy

RESULT:-

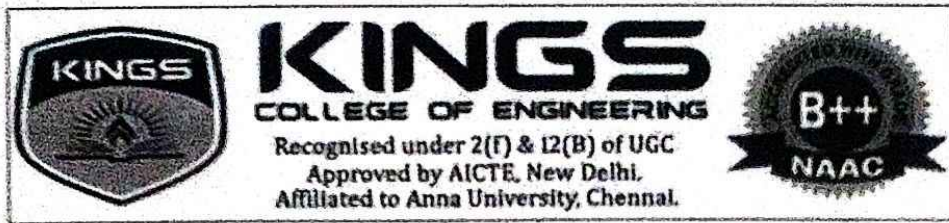Thus the load test on dc series motor was conducted and performance curves were drawn.



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
ACADEMIC YEAR :2022-2023 (ODD SEMESTER)

Course File

Format B

CONTENT BEYOND THE SYLLABUS

TITLE : Load Characteristics of DC Series
generators

OBJECTIVE : To draw the load Characteristics of
DC series generator by conducting load
test on it

METHODOLOGY : Experiment / Virtual lab.

EVALUATION : Questioning

DATE OF COMPLETION : 19/12/22

P. Nannayy

Staff Incharge Signature

Load Characteristics of DC series generator:

Aim:

To draw the load characteristics of DC series generator by conducting load test on it

Apparatus required:

| S.No | Apparatus required | Type | Range | Quantity |
|------|--------------------|-------------|----------------|----------|
| 1. | Ammeter | Moving coil | (0-20) amps | 1 |
| 2. | Voltmeter | Moving coil | (0-300) volts | 1 |
| 3. | Rheostat | wire wound | 2300, 1.7 amps | 1 |
| 4. | Resistive load | - | 3kw | 1 |
| 5. | Tachometer | Digital | - | 1 |
| 6. | Connecting wire | - | - | Required |

Formulae:

$$E_o = V + I_o R_o \text{ (volts)}$$

$$I_L = I_a + I_f \text{ (amps)}$$

$$R_a = V_o / I_a \text{ ohm}$$

Precaution:

- * All the above double single pole through (DPST) switch should be kept open
- * Motor field rheostat should be minimum position.
- * All the switches on resistive load should be in off position
- * In armature resistive, rheostat should be in maximum resistance position

Tabulation :

| S.no | Load current (amps) | Terminal voltage (V) | Generated voltage (V) |
|------|---------------------|----------------------|-----------------------|
| 1. | 1 A | 100V | 101.1 V |
| 2. | 2 A | 133V | 135.2 V |
| 3. | 3.3 A | 153V | 156.63V |
| 4. | 4.3 A | 170V | 174.73 V |
| 5. | 6 A | 183V | 189.6 V |
| 6. | 10 A | 205 V | 216 V |
| 7. | 12 A | 210 V | 223.2 V |


Model calculation:

$$E_g = V + I_a R_a$$

$$= 100 + (1 \times 1.1)$$

$$= 100 + 1.1$$

$$E_g = 101.1 \text{ V}$$

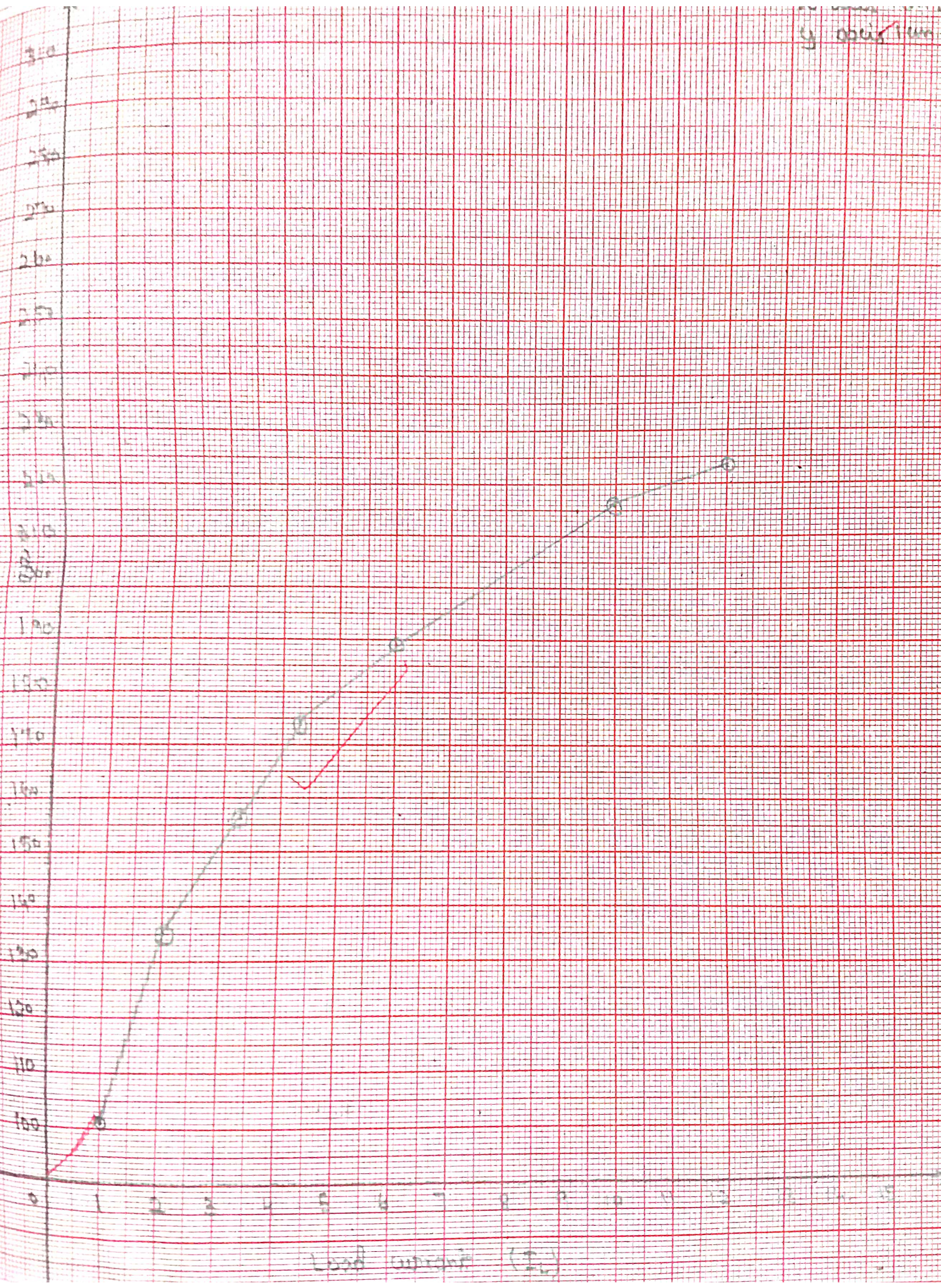

Procedure:

- * Make the condition as per the circuit diagram
- * Close the DPST switch 1
- * Start the motor using three point start
- * By adjusting motor field rheostat set the motor generator to its rated speed
- * Now close the DPST switch 2
- * Adjust the resistive load and note down corresponding load current I_L and terminal voltage indicated by ammeter and voltmeter respectively
- * Repeat the same procedure till load current reaches rated load current.

~~P. D. Denny~~

Result:

Thus the load test was conducted on DC series generator and the performance curve was drawn.

Teacher's Signature: